

C.U.SHAH UNIVERSITY

WADHWAN CITY

University (Winter) Examination -2013

Course Name :B.Tech Sem-I

Subject Name: - Fundamental of Electrical Engineering

Marks :70

Duration :- 2:30 Hours

Date : 20/12/2013

Instructions:-

- (1) Attempt all Questions of both sections in same answer book / Supplementary.
- (2) Use of Programmable calculator & any other electronic instrument is prohibited.
- (3) Instructions written on main answer Book are strictly to be obeyed.
- (4) Draw neat diagrams & figures (If necessary) at right places.
- (5) Assume suitable & Perfect data if needed.

SECTION – I

- | | |
|--|----|
| | 7 |
| Q.1 (a) State Ohm's law. | 1 |
| (b) Define Resistivity | 1 |
| (c) Define Magnetic flux density. | 1 |
| (d) Define Electric flux density. | 1 |
| (e) Define permittivity. | 1 |
| (f) State & Discuss Coulomb's law. | 2 |
| Q.2 (a) Derive the expression for delta to star conversion of resistive network. | 05 |
| (b) Define temperature co-efficient of resistance. Prove that $\alpha_t = \alpha_0 / (1 + \alpha_0 t)$. | 05 |
| (c) State and Explain the Kirchhoff's current and voltage laws. | 04 |
| OR | |
| Q.2 (a) Determine the equivalent resistance between the terminals A and B of network shown in figure 1. | 05 |

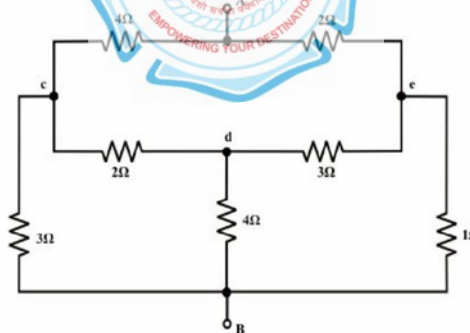


Figure 1

- | | | |
|---|--|----|
| | | 05 |
| (b) A coil has 25 ohm resistance at 40 ⁰ C and 45 ohm at 100 ⁰ C. Find its resistance and resistance temperature coefficient at 0 ⁰ C. | | 05 |
| (c) Explain effect of temperature on resistance of conductors, semiconductors and insulators. | | 04 |
| Q.3 (a) Derive equation for charging of capacitor in RC circuit. Also define time constant of circuit. | | 05 |
| (b) An iron ring of 40 cm mean diameter and 7cm ² cross section has an air gap of 2mm. it is informally wound with 750 turns of wire and carries a current of 3A. The iron takes 60% of the total mmf. Neglect magnetic leakage. Find the total mmf, magnetic flux, reluctance and flux density. | | 05 |
| (c) Explain Magnetic Hysteresis. | | 04 |

OR

- Q.3 (a) A parallel plate capacitor has a plate area of 4cm^2 . The plates are separated by three slabs of different dielectric materials of thickness 0.3, 0.4 & 0.3 mm with relative permittivities of 3, 2.5 and 2 respectively. Calculate the capacitance of each material and the voltage across them if the supply is 200v. 05
- (b) Derive the equation for the co-efficient of coupling of two magnetically coupled coils A and B. 05
- (c) Compare Electric and Magnetic circuits. 04

SECTION – II

- Q.4 (a) Define following terms in connection with A.C wave forms : 07
 (i) Frequency (ii) Phase difference (iii) Time Period
 (iv) form factor (v) Peak factor (vi) R.M.S. Value (vii) Average Value
- Q.5 (a) Prove that current through pure inductor is always lagging by 90° to its voltage and power consumed is zero. 05
- (b) Discuss resonance in R-L-C series circuits. Explain how pf, X_L and R vary with frequency. 05
- (C) State the effect of increase in Q on bandwidth. 04

OR

- Q.5 (a) Define the term (i) reactance (ii) inductive reactance (iii) capacitive reactance and explain how it depends on frequency in an A. C. circuit? 05
- (b) Three impedance $Z_1=5-j10F$, $Z_2=2+j20F$ and $Z_3=4+j2F$ are connected in parallel. If the total current is 20A, Find the current shared by each. 05
- (C) Compare series and parallel resonant circuits. 04
- Q.6 (a) Draw and explain the equivalent circuit of single phase transformer. 05
- (b) Draw and explain the vector diagrams when transformer is on ON-Load condition. 05
- (C) Three inductive coils, each having resistance of 15 ohm and an inductance of 0.03H connected in series, are connected 1. In star and 2. In delta to a 3 phase 400v, 50Hz supply. Calculate in each case line current and total power absorbed. 04

OR

- Q.6 (a) Explain the method of measuring 3- Φ power by two wattmeters. 05
- (b) Derive the relation between phase and line values of voltages and currents in balanced star connection. Draw complete phasor diagram of voltages and currents. 05
- (C) Derive the E.M.F equation of a transformer. 04

B**20***T*E*C*H****

