

**C.U.SHAH UNIVERSITY**

WADHWAN CITY

University (Winter) Examination -2013

Subject Name: -Computer Organization and Architecture

Course Name : B.Sc(I.T)/ BCA Sem-I

Duration :- 2:30 Hours

Date : 6/12/2013

**Instructions:-**

- (1) Attempt all Questions of both sections in same answer book / Supplementary.
- (2) Use of Programmable calculator & any other electronic instrument is prohibited.
- (3) Instructions written on main answer Book are strictly to be obeyed.
- (4) Draw neat diagrams & figures (If necessary) at right places.
- (5) Assume suitable & Perfect data if needed.

**SECTION - I**

- Q-1 Attempt the Following(Each Question content one marks) (7)
- (I) Write down the Definition of Gate
  - (II) What is Parity bit ? Explain it
  - (III) Draw the Circuit Diagram of Carry in Half Adder
  - (IV) What is Floating Point Representation ?
  - (V) Explain POS(Product Of Sum) with Example
  - (VI) Explain the Function of Control Unit.
  - (VII) What is Bollean Function?
- Q-2 (a) Which are the charteristics of Digital Computer . (5)
- Q-2 (b) Prove Demorgan's Law using Bollean Algebra (5)
- Q-2 (c) What is Computer ? Explain Block Diagram of Digital Computer (4)
- OR**
- Q-2(a) What is Binary Number System? Explain the Binary Conversion with Suitable Example (5)
- Q-2(b) What is Full adder ? Explain the Full adder with Diagram (5)
- Q-2(c) What is K' Map? Explain K' Map for two Variables with Example (4)
- Q-3 (a) What is Decoder ? Explain with Diagram (7)
- Q-3 (b) What is Mux? Explain with suitable Diagram (7)

**OR**

- Q-3(a) What is Endcoder ? Explain with Diagram (7)
- Q-3(b) Explain Don't Care Condition with suitable in K'MAP (7)

**SECTION – II**

- Q-4 : Answer the following questions (7)
- (a) Differentiate RAM and ROM (2)
  - (b) What is IO bus? (2)
  - (c) What is a binary counter? (2)
  - (d) Define: memory (1)
- Q- 5 Answer the following questions (14)
- (a) Explain RAM with block diagram and function table (5)
  - (b) List out various peripherals devices and Explain in brief (5)
  - (c) Describe NAND gate (4)

**OR**

- Q-5 Answer the following questions (14)
- (a) What is IO and memory bus? Differentiate IO and memory bus (5)
  - (b) Explain D flip flop in details (5)
  - (c) Describe EX-OR gate (4)
- Q-6 Answer the following questions (14)
- (a) What is stack? Explain register stack in details (7)
  - (b) What is CPU? Explain ALU with register set (7)

**OR**

- Q-6 Answer the following questions (14)
- (a) What is DMA? Explain DMA controller with block diagram (7)
  - (b) What is cache memory? Explain organization of cache memory (7)

\*\*\*\*\*6\*\*\*\*\*

