

**C.U.SHAH UNIVERSITY**

WADHWAN CITY

University (Winter) Examination -2013

Subject Name: -Basics Of Computer Architecture

Marks :70

Course Name:M.Sc(I.T) Sem-I

Duration :-2:30 Hours

Date :01/01/2014

**Instructions:-**

- (1) Attempt all Questions of both sections in same answer book / Supplementary.
- (2) Use of Programmable calculator & any other electronic instrument is prohibited.
- (3) Instructions written on main answer Book are strictly to be obeyed.
- (4) Draw neat diagrams & figures (If necessary) at right places.
- (5) Assume suitable & Perfect data if needed.

**SECTION-I****Q-1 Do As Directed (7)**

- (1) In Boolean Algebra  $A+A'=?$  and  $A.A'=?$  (1)
- (1) Convert  $(1024)_d=(\quad)_b$  where  $d$ =decimal , $b$ =Binary (2)
- (2) Find out the 2's Complement of  $(1000111)_b$  (2)
- (3)  $(1110001)_b + (1110011)_b=?$  (2)

Q-2 (a) What is a Gate ? Explain Various types of Gates in Digital Electronics. (5)

(b) Draw the Circuit diagram of Full Adder. (5)

(c) What is Computer ? Explain Block Diagram of Digital Computer (4)

**OR**

Q-2(a) What is Full Subtractor ? Explain in Brief. (5)

(b) Prove  $(ABC)'=A'+B'+C'$  and  $(A+B+C)'=A'B'C'$  (Demorgan's law) using Perfect Induction Method. (5)(c) Find out 9's Complement and 10's Complement of  $(108)_{\text{decimal}}$  (4)

Q-3 (a) Draw the Circuit diagram of following logical Expression (7)

(I)  $XYZ' + X'Y'Z + XY + X'Z$

(II)  $XY + X'Z + X(Y' + Z') + XZ$

(b) What is Decoder? Explain in brief (7)

**OR**

Q-3(a) Reduce the following logical expression using Boolean algebra (7)

$$(I) X'YZ(X'+X+Y)+X'Z'Y(XX'+Y+Z) + X'Z'(X'+XY+XY)$$

$$(II) X'(X'+Y+Y')+XZ(XY'+Y'+X')+X'Z$$

Q-3(b) What is Multiplexer ? Explain in brief. (7)

## SECTION-II

**Q-4 Do As Directed** (7)

(1) Draw the Circuit Diagram of Sum in Half Adder (2)

(2) Define Term : Memory (1)

(3) Define Term: Sequential Circuit (1)

(4) Convert (1056)<sub>10</sub> To Gray Code and XS-3 Gray Code (3)

Q-5 (a) What is Counter? Explain Binary Counter in brief. (5)

(b) What is Stack ? Explain Stack Organization in brief. (5)

(c) Draw the Circuit Diagram of following logical Expression (4)

$$XYZ+X'(YZ+ZX)+XY'+XZ+XY+Z$$

**OR**

Q-5 (a) What is addressing Modes ? Explain in brief (5)

(b) What is instruction? Explain Zero and one address instruction (5)

(c) What is Control Unit ? Explain in brief. (4)

Q-6 (a) What is Flip-Flop ? Explain S-R Flipflop with Truth- Table and Circuit Diagram (7)

(b) (i) Differentiate RAM Versus ROM (7)

(ii) What is Cache Memory ? Explain in brief.

**OR**

Q-6 (a) What is Register? Explain Types of Register . (7)

(b) What is DMA ? Explain in brief. (7)

\*\*\*\*\*01\*14\*\* \*\*\*\*\*

