

Enrollment No:-_____

Exam Seat No:-_____

C.U.SHAH UNIVERSITY

Summer-2015

Subject Code: 4TE03AEC1

Subject Name: Analog Electronic Circuit

Course Name: B.TECH(EEE/IC/EE)

Date :5/5/2015

Semester: 3

Marks: 70

Time: 2:30 To 5:30

Instructions:

- 1) Attempt all Questions of both sections in same answer book/Supplementary.
- 2) Use of Programmable calculator & any other electronic instrument prohibited.
- 3) Instructions written on main answer book are strictly to be obeyed.
- 4) Draw neat diagrams & figures (if necessary) at right places.
- 5) Assume suitable & perfect data if needed.

SECTION-I

Q-1

- (a) Why short circuit protection is required in ICs. 2
- (b) Explain diode regulators. 3
- (c) Write Full Form of 1. SMPS 2.BJT 2

Q-2

- (A) Describe analysis of single stage fet amplifier with necessary equations. 7
- (b) write a short note on tuned filter 7

OR

Q-2

- (A) Draw and explain Hybrid frequency model for CE configurations with necessary equations. 7
- (B) Draw and explain darlington pair configuration. 7

Q-3

- (A) Draw and explain class A amplifier with necessary equations. 7
- (B) Draw and Explain class AB amplifier with necessary equations. 7

OR

Q-3

- (A) Draw and explain class B amplifier with necessary equations. 7
- (B) Draw and explain Push Pull amplifier with necessary equations. 7



SECTION-II

- Q-4
- (A) Explain negative feedback for OPAMP. 2
- (B) Define terms : 1.Voltage Gain 2.Current Gain 2
- (c) Draw pin diagraph of IC741 (OPAMP) 2
- (d) Why heat sink is required in ICs? 1

- Q-5
- (A) Draw and explain non inverting amplifier with necessary equations. 7
- (B) Draw and explain ideal charteristic of OPAMP. 7

OR

- Q-5
- (A) Draw and explain inverting amplifier with necessary equations. 7
- (B) Explain any one balancing technquie for frequency compensation. 7

- Q-6
- (a) Explain working of Weinbridge oscillator with suitable diagram. 7
- (b) descirbe R.C. phase shift oscillllator with suitable diagram. 7

OR

- Q6
- (a) Explain working of Hartley oscillator with suitable diagram 7
- (b) Describe colpitts oscillator with suitable diagram. 7

