

# C U SHAH UNIVERSITY

## WADHWAN CITY

**Branch:** Electrical Engineering/ Electrical & Electronics Engineering

**Semester:** IV

**Subject Name:** Electrical & Electronics Measurement

**Subject Code:** 4TE04EEM1

### SECTION-I

- Q-1** (A) Define: 5  
1). Transformation ratio 2). Energy 3). Accuracy 4). Precision 5) Burden
- (B) A wattmeter having a range 1000 W has an error of  $\pm 1\%$  of full scale deflection. If the true power is 100 W, what would be the range of readings? 2
- Q-2** (A) How maxwell's bridge can be used to measure self inductance? Explain with circuit diagram. 4
- (B) What are incremental inductance and permeability? Describe how they are measured with Owen's bridge. 5
- (C) A resistance of approximate value of  $80\Omega$  is to be measured by voltmeter-ammeter method using a 1 A ammeter having a resistance of  $2\Omega$  and a 50 V voltmeter having a resistance of  $5000\Omega$ ,  
(a) Suggest which one of the two methods should be used? 5  
(b) Supposing in the suggested method the following measurements are made:  $I = 0.42$  A and  $V = 3.5$  V.  
What is the resulting error if the accuracy of the instruments is  $\pm 0.5\%$  at full scale and the errors are standard deviations?

### OR

- Q-2** (A) Explain Kelvin's double bridge method to find out low resistance. 4  
(B) Explain the absolute Null method for testing of a potential transformer. 5  
(C) Write short note on AC magnetic testing. 5
- Q-3** (A) What are the different sources of errors in a.c. bridges? Explain the precautions taken and the techniques used to eliminate these errors. 7  
(B) Explain construction of current transformer. List out causes of errors in current transformers. 7

### OR

- Q-3** (A) Explain the construction and working of magnetic potentiometer in detail. 7  
(B) Explain Hay's bridge with advantages and disadvantages. 7

### SECTION-II

- Q-4** 1). How to extend the range of given ammeter? 7

# C U SHAH UNIVERSITY

## WADHWAN CITY

- 2). What is the unit of energy measured by energy meter?
- 3). Transformer rating can be given in which unit?
- 4). Define power factor.
- 5). Explain the difference between capacitor and capacitance.
- 6). What is the use of De Sauty's Bridge?
- 7). What is the color code of 1 K $\Omega$  resistor?

- Q-5** (A) Explain frequency selective wave analyzer with block diagram. Also draw characteristics of active filter. **7**
- (B) Draw and explain basic instrumentation amplifier with applications. **7**

**OR**

- Q-5** (A) Explain the term "total Harmonic Distortion". Describe the functioning of a total harmonic distortion meter. **7**
- (B) Draw and explain block diagram of Cathode ray oscilloscope (CRO) in brief. **7**

- Q-6** (A) Explain Lissjous patterns for Phase and frequency measurement. **7**
- (B) For Power measurement explain Dynamometer type instrument with neat diagram. **7**

**OR**

- Q-6** (A) Describe the Murray Loop test for localization of ground and short circuit faults in cables. **7**
- (B) Classify systematic errors. Discuss each in detail. **7**