

Enrollment No:- _____

Exam Seat No:- _____

C.U.SHAH UNIVERSITY

Summer-2015

Subject Code: 4TE03AEL1

Subject Name: Advance Electronics

Course Name: B.TECH(EC)

Date :5/5/2015

Semester: 3

Marks: 70

Time: 2:30 To 5:30

Instructions:

- 1) Attempt all Questions of both sections in same answer book/Supplementary.
- 2) Use of Programmable calculator & any other electronic instrument prohibited.
- 3) Instructions written on main answer book are strictly to be obeyed.
- 4) Draw neat diagrams & figures (if necessary) at right places.
- 5) Assume suitable & perfect data if needed.

SECTION I

Q-1 Define and formulate the following.

- | | |
|-----------------------------|---|
| a) Voltage Series Feedback | 2 |
| b) Voltage Stability Factor | 2 |
| c) Input resistance | 2 |
| d) Voltage Shunt Feedback | 1 |

Q-2 Attempt all.

- | | |
|---|---|
| a) Explain Thevenin's theorem with help of example. | 5 |
| b) Define: h-Parameters with help of example. | 5 |
| c) Explain Emitter Follower. Enlist technical features. | 4 |

OR

Q-2

- | | |
|---|---|
| a) Explain Norton's theorem. | 5 |
| b) Explain FET Small-Signal Model. | 5 |
| c) Compare various Transistor Amplifier Configurations. | 4 |

Q-3

- | | |
|---|---|
| a) Draw and explain Crystal Oscillators | 5 |
| b) Describe classification of Amplifiers and Distortion in Amplifiers | 5 |
| c) Define: Thermal runaway and Thermal stability | 4 |

OR

Q-3

- | | |
|--|---|
| a) What is FET Small-Signal Model? Explain it. | 5 |
| b) Explain Hybrid -pi CE Transistor Model | 5 |
| c) Draw RC Coupled Amplifier. Explain | 4 |



SECTION II

- Q-4 Define and formulate the following.**
- a) The operating point 2
 - b) Barkhausen Criterion 2
 - c) Bode Plots 2
 - d) Ideal operational Amplifier 1
- Q-5** **14**
- a) Explain Class A large Signal Amplifiers 5
 - b) Explain Push-Pull Amplifiers 5
-
- c) Draw and explain Phase-Shift Oscillator 4

OR

- Q-5** **14**
- a) Explain Transformer Coupled Audio Power Amplifier. 5
 - b) Explain Class B Amplifiers. 5
 - c) What is Second Harmonic Distortion? Discuss. 4
- Q-6** **14**
- a) Explain Series Voltage Regulator. 5
 - b) Draw and explain Hartley Oscillator. 5
 - c) Draw and explain Differential Amplifier. 4

OR

- Q-6** **14**
- a) Draw and explain Wien Bridge Oscillator. 5
 - b) Explain Negative Feedback Amplifiers. 5
 - c) Explain Emitter-Coupled Differential Amplifier. 4

