

C.U.SHAH UNIVERSITY

Summer-2015

Subject Code: 4TE03DEL1 **Subject Name: Digital Electronics**

Course Name: B.Tech (CE,EC)

Date: 7/5/2015

Semester:III

Marks: 70

Time:02:30 TO 05:30

Instructions:

- 1) Attempt all Questions of both sections in same answer book/Supplementary.
- 2) Use of Programmable calculator & any other electronic instrument prohibited.
- 3) Instructions written on main answer book are strictly to be obeyed.
- 4) Draw neat diagrams & figures (if necessary) at right places.
- 5) Assume suitable & perfect data if needed.

SECTION-I

Q-1 (a) What is gate ? Explain types of gate with truth table and diagram. (7)

Q-2 (a) Prove that NAND and NOR GATE are universal gates with the help of diagram. (7)

(b) what is complement ? Explain 1's and 2's complement with example. (7)

OR

(a) What is POS and SOP ? Explain with suitable examples. (7)

(b) Explain Full adder with circuit diagram. (7)

Q-3(a) Explain Excess-3 Code and generate Excess-3 Code for numbers 0-9 (7)

(b)What is K'MAP ? Explain 2 variable and 4 variable K'MAP with example. (7)

OR

(a) Design a combination circuits for full subtractor (7)

(b) Explain binary to octal convertor (Decoder)with the help of diagram. (7)

SECTION-II

Q-4 (a) Explain demultiplexer with suitable diagram (7)

Q-5(a) What is Flipflop ? Explain Master Slave J-K Flip flop with truth table and diagram(7)

Q-5(b) What is Flipflop ? Explain S R Flip flop with truth table and diagram (7)

OR

(a) Design octal to binary encoder. (7)

(b) Write a note on Register. (7)

Q-6(a) Explain Binary ripple counter. (7)

(b) Explain 7's and 9's complement with example. (7)

OR

(a) What is multiplexer? Explain with the help of diagram (7)

(b) Explain T flip flop with diagram and truth table. (7)

