

**C U SHAH UNIVERSITY**  
**FACULTY OF TECHNOLOGY AND ENGINEERING**

**SUMMER EXAMINATION 2015**

**Branch:** Electronics and Communication  
**Subject Code:** 4TE04ACM1  
**Total marks :** 70

**Semester:** 4  
**Subject Name:** Analog Communication

**Instructions:**

1. The question paper comprises two sections.
2. Draw neat figures wherever required.

**SECTION – I**

- Q - 1 Answer the questions below. [07]**
- a. What is flicker noise?
  - b. Describe the term adjacent channel selectivity.
  - c. What is skin effect?
  - d. Draw diagram of parallel tuned circuit and give equation of parallel impedance.
  - e. Define Q-factor.
  - f. Why modulation in communication is required?
  - g. What is the requirement of image rejection in communication receivers?
- Q – 2.a The equivalent noise resistance for an amplifier is  $300 \Omega$  and the equivalent shot noise current is  $5 \mu\text{A}$ . The amplifier is fed from  $150\Omega$ ,  $10\mu\text{V}$  rms sinusoidal signal source. Calculate the individual noise voltages at the input and the input signal-to-noise (SNR) in decibels. The noise bandwidth is 10 MHz [04]**
- Q – 2.b Answer any two questions. [10]**
- (i) Derive the noise factor for cascade amplifiers.
  - (ii) Explain super heterodyne receiver tracking methods
  - (iii) Derive the equation of 3-dB bandwidth in respect to frequency selection of tuned circuit.
- Q - 3 .a The RC load for a diode detector consists of  $1000\text{pF}$  capacitor in parallel with  $10\text{k}\Omega$  resistor. Calculate the maximum modulation depth that can be handled for sinusoidal modulation at a frequency of  $10\text{kHz}$  if diagonal peak clipping is to be avoided. [04]**
- Q – 3.b Answer any two questions. [10]**
- (i) Describe any one type of amplitude demodulator circuits.
  - (ii) Using neat sketch describe BJT collector modulator circuit.
  - (iii) Describe pre-emphasis and de-emphasis

**SECTION – II****Q - 4 Answer the question below.**

- a. What is the benefit of SSBSC modulation over SSB modulation [01]
- b. Draw basic diode envelope detector circuit and output voltage waveform [02]
- c. Mention the significance of modulation index. [02]
- d. Mention secant law in respect to maximum usable frequency of skywave propagation. [02]
- Q – 5.a** Draw figure of superheterodyne receiver. [04]
- Q – 5.b** Explain the indirect method of generating FM signal [05]

**OR**

- Q – 5.b** Describe any one type of balanced modulators. [05]
- Q – 5.c** Describe Phasing method for SSB Generation. [05]

**OR**

- Q – 5.c** Draw and explain block diagram of frequency stabilized FM oscillator. [05]
- Q – 6.a** Describe sinusoidal frequency modulation. Derive equation of modulation index ( $\beta$ ) for FM. [04]
- Q – 6.b** Provide the equation of field strength at a distance (d) from surface wave propagation. [05]  
Describe surface wave propagation.

**OR**

- Q – 6.b** Describe Varactor diode Phase modulator. [05]
- Q – 6.c** In respect to sky wave propagation provide brief contribution of D Layer, E Layer, E<sub>s</sub> Layer, F<sub>1</sub> Layer and F<sub>2</sub> Layer [05]

**OR**

- Q – 6.c** Derive equation of average power in sinusoidal FM. Provide equation of Carson's rule for Non-sinusoidal modulation. [05]

\*\*\*