



- Q-3 A. Obtain an expression for the equivalent star network resistance for a given delta network resistances. 07
- B. Derive the expression of inductance for the coupled coil connected in series. 07

OR

- Q-3 A. An iron ring having a cross sectional area of 5 cm x 4 cm, a mean diameter of 18 cm has a coil of 270 turns uniformly wound over it. A current of 1.27 A flows through the coil which produces a flux of 1.13 mWb in the ring. Find the reluctance of the circuit, the absolute permeability of Iron. 07
- B. Derive the expression for Energy stored in a charged capacitor. 07

**SECTION-II**

- Q-4 A. Define following terms with respect to A.C. waveform 04  
 (i) R.M.S. value (ii) Power factor  
 (iii) Peak factor (iv) Form Factor 03

- B. Draw the clear A.C. waveform. Label time period, X and Y axes for voltage and time, and peak to peak values.

- Q-5 A. Prove that current in pure inductive circuit lags its voltage by  $90^0$  05
- B. Give the advantages of three phase system over single phase system. 05
- C. Find the capacitance which must be connected in series with a 100 W, 110 V lamp in order that the lamp may draw its normal current when the combination is connected to a 230 V, 50 Hz supply. 04

OR

- Q-5 A. Prove that for purely capacitive circuit current be leading  $90^0$  to applied voltage. 05
- B. What are the various electrical losses in a transformer? Explain them. 05
- C. An alternating current having an equation  $I = 60\sin 314t$ . 04  
 Find: (i) Maximum value of current (ii) Frequency



- Q-6 A. A voltage of 125 V at 50 Hz is applied across a non inductive resistor connected in series with a condenser. The current in the circuit is 2.2 A the power loss in the resistor is 96.8 W and that in condenser is negligible. Calculate the values of resistances and capacitances. 07
- B. Explain the working principle and construction of a transformer. 07
- OR
- Q-6 A. Calculate 1) form factor 2) peak factor of a full wave rectified sine wave. 07
- B. Prove that RMS value of a sinusoidal current is  $0.707 I_m$ . 07

