

Enrollment No:-\_\_\_\_\_

Exam Seat No:-\_\_\_\_\_

## C.U.SHAH UNIVERSITY

### Summer-2015

Subject Code: 2TE01BEE1    Subject Name: Basic Electrical Engineering

Course Name:DIPLOMA

Date: 8/5/2015

Semester:I

Marks: 70

Time:10:30 TO 01:30

---

**Instructions:**

- 1) Attempt all Questions of both sections in same answer book/Supplementary.
  - 2) Use of Programmable calculator & any other electronic instrument prohibited.
  - 3) Instructions written on main answer book are strictly to be obeyed.
  - 4) Draw neat diagrams & figures (if necessary) at right places.
  - 5) Assume suitable & perfect data if needed.
- 

Q1.Do as directed (14)

- (a) Define 'Current' .
- (b) Draw circuit symbols of resistor and inductor.
- (c) Write the units of capacitance and Inductance.
- (d) Write Joule's law of electric heating.
- (e) Define frequency and write unit of frequency.
- (f) Write unit of resistivity.
- (g) Write formula for Resonance Frequency.
- (h) What is relation between line voltage and phase voltage in Star connection.
- (i) What is the function of Commutator in DC generator?
- (j) Why starter is used in motor?
- (k) Write the name of two types of induced EMF..
- (l) What should be the resistance of long wire, low or high?
- (m) Write formula for Ohm's law.
- (n) Write function of resistor and capacitor.

**Attempt any four**

Q2. (a) Define resistance and explain factors affecting on resistance of conductor. (7)  
(b) Derive equations for resistors in series and resistors in parallel. (7)

Q3. (a) Define capacitance and explain factor affecting on capacitance . (7)  
(b) Derive equations for capacitor in series and capacitors in parallel. (7)

Q4. (a) Define electromagnetic induction and explain Faraday's laws of induction. (7)  
(b) Define magnet and Explain magnetic hysteresis loop . (7)



Q5. (a) Explain generation of AC voltage and current. (7)  
(b) Explain AC through pure & alone resistor. (7)

Q6.(a) Explain star and delta connection. (7)  
(b) Derive relation between line current and phase current in Delta connection. (7)

Q7.(a) Explain construction and working of DC generator. (7)  
(b) Explain construction and working of single phase transformer.  
(7)

Q8.(a) Explain Kirchhoff's current law(KCL) and voltage law(KVL). (7)  
(b) Explain construction and working of MCB and ELCB. (7)

.....



- પ્ર-1 માંગ્યા પ્રમાણે લખો. (14)  
 (એ) કરંટ ની વ્યાખ્યા લખો.  
 (બી) રેસીસ્ટર અને ઈન્ડક્ટર ના સરકીટ સીભોલ દોરો.  
 (સી) કેપેસીટંસ અને ઈન્ડક્ટંસ ના એકમો લખો.  
 (ડી) ઈલેક્ટ્રીક હીટીગ માટેનો જુલો નિયમ લખો.  
 (ઇ) ફીકવંસી ની વ્યાખ્યા અને તેનો એકમ લખો.  
 (એફ) રેજિસ્ટીવીટી નો એકમ લખો.  
 (જી) રેજોનંસ ફીકવંસી નું સુત્ર લખો.  
 (એચ) સ્ટાર કનેક્શન માં લાઈન વોલ્ટેજ અને ફૈજ વોલ્ટેજ વચ્ચેનો સબંધ શું છે?  
 (આઈ) ડીસી જનરેટર માં કોમ્યુટેર નું કાર્ય શું છે?  
 (જે) મોટર માં સ્ટાર્ટર શા માટે ઉપયોગ થાય છે.?  
 (કુ) ઈન્જ્યુસડ ઈ.એમ.એફ. ના બે પ્રકારના નામ લખો.  
 (એલ) લાંબા વાયર નો રેજિસ્ટંસ શું હોવો જોઈએ, ઓછો કે વધારે?  
 (એમ) ઓહમ ના નિયમ નું સુત્ર લખો.  
 (એન) રેજિસ્ટર અને કેપેસીટર નું કાર્ય લખો.

### કોઈ પણ ચાર પ્રશ્નો ના જવાબ લખો.

- પ્ર-2 (એ) રેજિસ્ટંસ ની વ્યાખ્યા લખો અને કન્ડક્ટર ના રેજિસ્ટંસ ઉપર અસર કરતા પરીબળો સમજાવો. (7)  
 (બી) રેજિસ્ટર ના શ્રેષ્ઠી અને સમાંતર જોડાણ માટે ના સુત્ર મેળવો. (7)
- પ્ર-3 (એ) કેપેસીટંસ ની વ્યાખ્યા લખો અને કેપેસીટંસ ઉપર અસર કરતા પરીબળો સમજાવો. (7)  
 (બી) કેપેસીટર ના શ્રેષ્ઠી અને સમાંતર જોડાણ માટે ના સુત્ર મેળવો. (7)
- પ્ર-4 (એ) ઈલેક્ટ્રોમેગનેટીક ઈન્ડક્શન ની વ્યાખ્યા લખો અને ફેરેડ ના ઈલેક્ટ્રોમેગનેટીક ઈન્ડક્શન ના નિયમો સમજાવો. (7)  
 (બી) મેગનેટ ની વ્યાખ્યા લખો અને મેગનેટીક હીસટરેસીસ લુપ સમજાવો. (7)
- પ્ર-5 (એ) એસી વોલ્ટેજ અને કરંટ નું જનરેશન સમજાવો. (7)  
 (બી) શુધ્ય અને એકલા રેજિસ્ટર માં એસી સમજાવો. (7)
- પ્ર-6 (એ) સ્ટાર અને ડેલ્ટા કનેક્શન સમજાવો. (7)  
 (બી) ડેલ્ટા કનેક્શન માં લાઈન અને ફૈજ કરંટ વચ્ચેનો સબંધ મેળવો (7)
- પ્ર-7 (એ) ડીસી જનરેટર ની રચના અને કાર્ય સમજાવો (7)  
 (બી) ટ્રાંસફોર્મર ની રચના અને કાર્ય સમજાવો. (7)
- પ્ર-8 (એ) કીર્ચોફ ના કરંટ અને વોલ્ટેજ ના નિયમો સમજાવો. (7)  
 (બી) એમ.સી.બી અને ઈ.એલ.સી.બી ની રચના અને કાર્ય સમજાવો. (7)

