

C.U.SHAH UNIVERSITY

Winter Examination-2015

Subject Name: Linear Electronics

Subject Code: 4TE03LNE1

Branch: B.Tech (CE)

Semester: 3

Date:5/12/2015

Time:2:30 To 5:30

Marks :70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1 Attempt the following questions:

(14)

- a) Why are the h parameters preferred to analyze a circuit using BJT?
- b) Why is a hybrid model of transistor preferred over other models?
- c) What is the use of class C amplifiers?
- d) Why is a power amplifier called large signal amplifier?
- e) What are the practical applications of emitter follower?
- f) What is the effect of negative feedback on bandwidth of an amplifier?
- g) What will be the output shape of an op-amp differentiator with sinusoidal and square wave input?
- h) What will be the output shape of an op-amp integrator with sinusoidal and square wave input?
- i) What are the applications of op-amp integrators?
- j) Why is an emitter follower called so?
- k) What are the different types of feedback?
- l) What do you understand by feedback in an amplifier?
- m) Why do we use transformer in the output stage of power amplifier?
- n) Give the differences between voltage and power amplifiers.

Attempt any four questions from Q-2 to Q-8

Q-2 Attempt all questions

(14)

- (a) Draw the h-parameter equivalent circuit of Common Emitter Amplifier circuit and derive the expression for input impedance, output impedance, voltage gain and current gain.
- (b) Show that maximum collector efficiency of class A transformer coupled power amplifier is 50%.



