



**B** Design a 4 bit BCD to Gray code converter.

**Q-5** **Attempt all questions** (14)

**A** What is meant by multiplexer? Explain with diagram and truth table the Operation of 4-to-1 line multiplexer.

**B** What is meant by decoder? Explain 3-to-8 line decoder with diagram and truth table.

**Q-6** **Attempt all questions** (14)

**A** Explain D type positive edge triggered flip flop.

**B** Explain the working of the Master Slave J K flip-flop with necessary logic diagram.

**Q-7** **Attempt all questions** (14)

**A** With neat diagram explain the operation of 4- bit serial- in-serial –out register. Draw the timing diagram and give its truth table.

**B** With necessary sketch explain bi-directional shift register with parallel load.

**Q-8** **Attempt all questions** (14)

**A** Explain the working of 4 bit asynchronous up counter.

**B** Describe the Comparison of Counters with Registers.

