

# C.U.SHAH UNIVERSITY

## Winter Examination-2015

**Subject Name: Operational Amplifier**

**Subject Code: 5SC03PHE1**

**Branch: M.Sc.(Physics)**

**Semester: 3**

**Date: 05/12/2015**

**Time: 2:30 To5:30**

**Marks: 70**

**Instructions:**

- (1) Use of Programmable calculator and any other electronic instrument is prohibited.
  - (2) Instructions written on main answer book are strictly to be obeyed.
  - (3) Draw neat diagrams and figures (if necessary) at right places.
  - (4) Assume suitable data if needed.
- 

### SECTION – I

- Q-1 Attempt the Following questions (07)**
- a. Define CMRR. **02**
  - b. Draw Schematic symbol of Op-Amp. **02**
  - c. Define input offset voltage. **02**
  - d. Define Slew rate? **01**
- Q-2 Attempt all questions (14)**
- a) Explain open loop Op-Amp configurations. **05**
  - b) Explain in details Differential amplifier with one Op-amp. **05**
  - c) Draw and explain equivalent circuit of Op-Amp in details. **04**
- OR**
- Q-2 Attempt all questions (14)**
- a) Explain the open-loop voltage gain as a function of frequency. **05**
  - b) Explain differentiator in details. **05**
  - c) Explain in details peaking amplifier. **04**
- Q-3 Attempt all questions (14)**
- a) Draw the circuit of basic integrator using an op-amp. What are the problems associated with this configuration? How can they be overcome? **07**
  - b) Derive the expression for voltage gain, input resistance, output resistance and bandwidth of a non-inverting amplifier with feedback using op-amp with voltage Series feedback. **07**
- OR**
- Q-3 Attempt all questions (14)**
- a) Explain application of op-amp (Inverting configuration) as summing, scaling and averaging circuit. **07**
  - b) Derive the expression for voltage gain, input resistance, output resistance and bandwidth of an inverting amplifier using op-amp with negative voltage shunt feedback. **07**



## SECTION – II

<b>Q-4</b>	<b>Attempt the Following questions</b>	<b>(07)</b>
	<b>a.</b> What are the differences between active and passive filters	<b>02</b>
	<b>b.</b> Give the types of oscillators.	<b>02</b>
	<b>c.</b> Give the important characteristics of comparators.	<b>02</b>
	<b>d.</b> What is PLL?	<b>01</b>
<b>Q-5</b>	<b>Attempt all questions</b>	<b>(14)</b>
	<b>a)</b> Explain working and application of 555 IC based Astable multivibrator.	<b>05</b>
	<b>b)</b> Write a short note on peak detector.	<b>05</b>
	<b>c)</b> Explain Basic comparator in details.	<b>04</b>
	<b>OR</b>	
<b>Q-5</b>	<b>Attempt all questions</b>	<b>(14)</b>
	<b>a)</b> Draw and explain the block diagrams of 555 Timer.	<b>05</b>
	<b>b)</b> Write a short note on Schmitt Trigger.	<b>05</b>
	<b>c)</b> Explain phase shift oscillator with help of suitable figure and waveforms.	<b>04</b>
<b>Q-6</b>	<b>Attempt all questions</b>	<b>(14)</b>
	<b>a)</b> Explain in details 555 IC based Monostable multivibrator.	<b>07</b>
	<b>b)</b> Discuss the fixed voltage regulator and adjustable voltage regulator with necessary circuit diagram.	<b>07</b>
	<b>OR</b>	
<b>Q-6</b>	<b>Attempt all Questions</b>	<b>(14)</b>
	<b>a)</b> Explain in details Positive and Negative Clippers.	<b>07</b>
	<b>b)</b> With the help of a circuit diagram, explain the operation of first order Low pass filter.	<b>07</b>

