

# C.U.SHAH UNIVERSITY

## Summer Examination-2016

**Subject Name: Network Analysis**

**Subject Code: 4TE03NAS1**

**Branch: B. Tech (EC)**

**Semester: 3**

**Date: 26/04/2016**

**Time: 02:30 To 05:30**

**Marks: 70**

**Instructions:**

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
- (2) Instructions written on main answer book are strictly to be obeyed.
- (3) Draw neat diagrams and figures (if necessary) at right places.
- (4) Assume suitable data if needed.

**Q-1 Define the following terms: (14)**

- a) Circuit.
- b) Network.
- c) Node.
- d) Junction.
- e) Passive network.
- f) Active network.
- g) Independent source.
- h) Dependent source.
- i) Graph
- j) Tree
- k) Incident matrix


**State the following theorems:**

- l) State the Thevenin's theorem
- m) State the Norton's theorem.
- n) State the reciprocity theorem.

**Attempt any four questions from Q-2 to Q-8**

**Q-2 Attempt all questions (14)**

- (a) Determine the current through  $4\Omega$  resistor branch of the network given in Fig-1 using mesh analysis. **09**

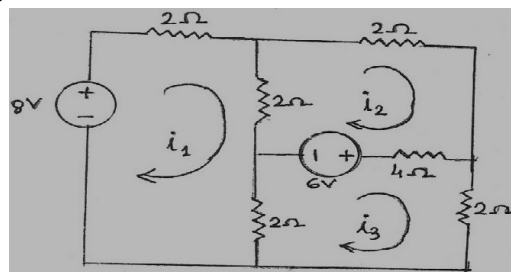

**Fig-1**



- (b) What are the relationship between voltage and current and voltage for R, L and C? Also mention the initial and final condition for R, L and C components in the different conditions. 05

Q-3

**Attempt all questions**

(14)

- (a) For the given network in Fig- 2, switch K is changed from position 1 to 2 at time  $t = 0$ . Find out the value of  $i$ ,  $di / dt$  and  $d^2i / dt^2$  at  $t = 0^+$ . Assume that steady state having been reached before switching. 07

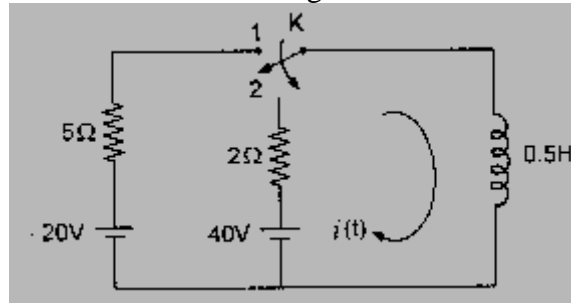


Fig -2

- (b) For the given network in Fig-3, switch k is closed at time  $t = 0$ . Find out the particular solution for the current  $i(t)$ . 07

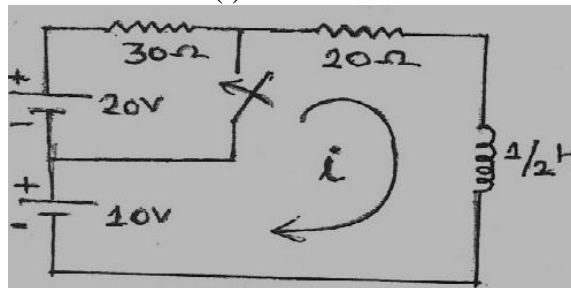


Fig - 3

Q-4

**Attempt all questions**

(14)

- (a) State the superposition theorem. Find the voltage across  $1k\Omega$  resistor in the circuit shown in Fig -4, using superposition theorem. 07

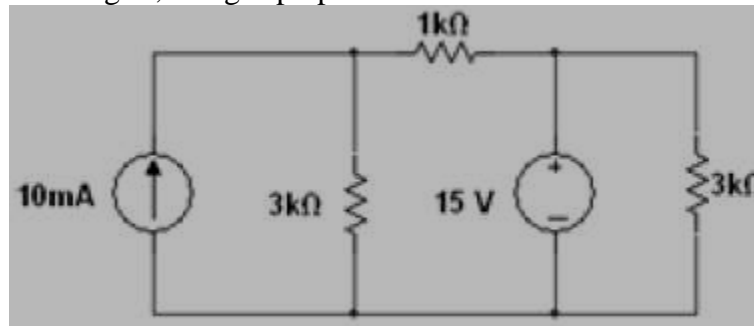


Fig -4

- (b) In the network of Fig.-5, the switch K is moved from position a to b at  $t=0$  (Steady state existing). Solve for the current  $i(t)$  using Laplace transformation method. Use  $R = 10\Omega$ ,  $L = 1H$ ,  $C = 1F$ . 07



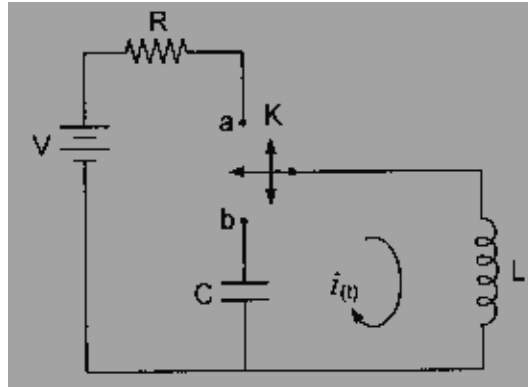


Fig -5

Q-5 **Attempt all questions** (14)

- (a) Explain the various types of Interconnections of the Two port networks in brief. 07
- (b) State and prove maximum power transfer theorem with suitable examples. 07

Q-6 **Attempt all questions** (14)

- (a) Derive the expression for z-parameters in terms of g -parameters and vice versa. 07
- (b) Find the z-parameters for the given network in Fig-6. 07

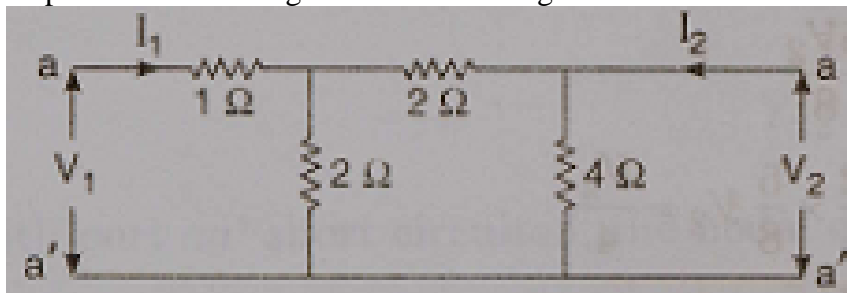


Fig -6

Q-7 **Attempt all questions** (14)

- (a) Write short note on series resonance 07
- (b) A 220v, 100Hz ac source supplies a series RLC circuit with a capacitor and a coil. If the coil has 50 mΩ resistance and 5 mH inductance, find, at a resonance frequency 100 Hz what is the value of capacitor. Also calculate the Q factor and half power frequencies of the circuit. 07

Q-8 **Attempt all questions** (14)

- (a) Explain the concept of poles and zeros and their significance.
- (b) Explain necessary conditions for driving-point functions

