

# C.U.SHAH UNIVERSITY

## Summer Examination-2017

**Subject Name : Electronics**

**Subject Code : 4SC04PHE1**

**Branch : B.Sc. (All)**

**Semester : 4**

**Date : 28/04/2017**

**Time : 10:30 To 01:30**

**Marks : 70**

**Instructions:**

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
- (2) Instructions written on main answer book are strictly to be obeyed.
- (3) Draw neat diagrams and figures (if necessary) at right places.
- (4) Assume suitable data if needed.

- Q-1          Attempt the following questions:          (14)**
- a) What do you mean by BJT?          01
  - b) Distinguish BJT and UJT.          01
  - c) JFET having \_\_\_\_\_ terminals.          01
  - d) Write advantages of UJT.          01
  - e) Write usefulness of JFET.          01
  - f) Draw schematic diagram of MOSFET.          01
  - g) What is transistor biasing? Why it becomes necessary for biasing purpose?          01
  - h) Which number system is found useful in digital electronics?          01
  - i) Define: stability factor.          01
  - j) Convert  $20.78125_{10}$  into binary number.          01
  - k) Calculate  $11001_2$  into decimal number.          01
  - l) Define: universal logic gates.          01
  - m) What is thermistor?          01
  - n) Distinguish analog and digital electronics.          01
- Attempt any four questions from Q-2 to Q-8**
- Q-2          Attempt all questions          (14)**
- a) What is transistor? How transistor biasing can be done through feedback resistor biasing method.          07
  - b) Discuss briefly base resistor biasing method. Write its merits and demerits.          07
- Q-3          Attempt all questions          (14)**
- a) Explain briefly JFET with its construction and working principle.          07
  - b) What is phase reversal process in transistor amplifier? - Discuss.          07
- Q-4          Attempt all questions          (14)**
- a) Distinguish JFET and BJT briefly.          07
  - b) What is MOSFET? Explain working of MOSFET.          07



<b>Q-5</b>	<b>Attempt all questions</b>	<b>(14)</b>
	a) How UJT works as a relaxation oscillator? Write its advantages.	07
	b) How transistor amplifier works practically? – Explain.	07
<b>Q-6</b>	<b>Attempt all questions</b>	<b>(14)</b>
	a) Discuss JFET parameters briefly.	07
	b) What is the physical significance of load line in transistor amplifier? Discuss its analysis.	07
<b>Q-7</b>	<b>Attempt all questions</b>	<b>(14)</b>
	a) Write short notes on (1) OR gate and (2) NOT gate.	07
	b) Discuss how AND, OR and NOT gate can be made through NAND gate.	07
<b>Q-8</b>	<b>Attempt all questions</b>	<b>(14)</b>
	a) For a given JFET, if a change in drain voltage of 4V produces a change in drain current of 0.06 mA. Calculate ac drain resistance.	04
	b) Discuss-Thermistor characteristics.	05
	c) Write short note on AND gate.	05

