

# C.U.SHAH UNIVERSITY

## Summer Examination-2017

**Subject Name: Linear Electronics**

**Subject Code: 4TE03LNE1**

**Branch: B.Tech (CE)**

**Semester: 3**

**Date: 27 /03/2017**

**Time: 10:30 To 01:30**

**Marks: 70**

**Instructions:**

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
- (2) Instructions written on main answer book are strictly to be obeyed.
- (3) Draw neat diagrams and figures (if necessary) at right places.
- (4) Assume suitable data if needed.

- Q-1 Attempt the following questions: (14)**
- |    |  |   |
|----|--|---|
| a) | Define Oscillator.   | 1 |
| b) | Define Input Offset Current.   | 1 |
| c) | Define Slew rate.  | 1 |
| d) | Define Operating Point.  | 1 |
| e) | Define Positive feedback.  | 1 |
| f) | If $A=100$ And $B=50\%$ . Then $A_f = \dots\dots\dots$ ?   | 1 |
| g) | If Operating Point is in Middle of Load Line Then amplifier is treated as<br>a.....<br>A) Class B. B) Class A. C) Class C. D) Class D.             | 1 |
| h) | In push pull circuit each transistor conducts for .....<br>A) $90^\circ$ . B) $180^\circ$ . C) $270^\circ$ . D) $360^\circ$ .                      | 1 |
| i) | In oscillator feedback loop may contain<br>A) L and C. B) R and C. C) crystal. D) all of above   | 1 |
| j) | If $AB=1$ then oscillation is called .....oscillation<br>A) Damped. B) Under damped C) over damped D) critically damped.                           | 1 |
| k) | If $B=1$ and $A=100$ then $f_2f_1 = \dots\dots\dots$ Hz.<br>A) $100f_2$ B) $f_2$ C) $f_2/2$ D) $101f_2$  | 1 |
| l) | To achieve $180^\circ$ out of phase signal, input should be applied to pin no.....of<br>IC741.<br>A) 3 B) 2. C) 4. D) 5.                           | 1 |
| m) | Ideal op amp has very low .....<br>A) Output impedance B) gain C) Input impedance. D) bandwidth  | 1 |
| n) | The thickness of Base of power transistor is.....as compare to ordinary<br>transistor<br>A) Thick B) thin C) same (b) depend on construction style | 1 |



**Attempt any four questions from Q-2 to Q-8**

<b>Q-2</b>	<b>Attempt all questions</b>	<b>(14)</b>
1.	What IS feedback? Draw general block diagram of it. And derive the equation for overall gain with feedback..	<b>06</b>
2.	Compare Positive feedback and negative feedback.	<b>03</b>
3.	Explain the advantages of feedback.	<b>05</b>
<b>Q-3</b>	<b>Attempt all questions</b>	<b>(14)</b>
1.	Draw and Explain the working of Hartley Oscillator.	<b>06</b>
2.	Design oscillator which produce frequency of 5 K Hz using a Collpits oscillator	<b>04</b>
3.	Give the classification of oscillation. State the need of oscillation. .	<b>04</b>
<b>Q-4</b>	<b>Attempt all questions</b>	<b>(14)</b>
1.	Draw pin diagram of IC 741. State function of each pin. State the ideal characteristic of it	<b>06</b>
2.	Define CMRR. If CMRR= 100 and $A_{cm}= 10$ then find the value of output voltage $V_{in}=10mV$	<b>04</b>
3.	Draw and Explain OP amp As an integrator.	<b>04</b>
<b>Q-5</b>	<b>Attempt all questions</b>	<b>(14)</b>
1.	Explain distortion if power amplifier.	<b>04</b>
2.	Compare power amplifier and voltage amplifier.	<b>04</b>
3	Explain Push Pull amplifier in detail.	<b>06</b>
<b>Q-6</b>	<b>Attempt all questions</b>	<b>(14)</b>
1.	Explain voltage divider biasing method.	<b>04</b>
2.	Explain Emitter Follower for small signal.	<b>04</b>
3.	Explain Two-Port Devices and the Hybrid Model.	<b>04</b>
4.	Define biasing. State the types of biasing.	<b>02</b>
<b>Q-7</b>	<b>Attempt all questions</b>	<b>(14)</b>
1.	Draw and explain voltage series feedback with necessary equation.	<b>06</b>
2.	Draw and explain Phase-Shift Oscillator.	<b>04</b>
3.	Explain Inverting and non inverting op-amp.	<b>04</b>
<b>Q-8</b>	<b>Attempt all questions</b>	<b>(14)</b>
1.	An amplifier has a gain 100 without feedback and cutoff frequency are $f_1=1$ KHz and $f_2=500$ KHz. If 1% output voltage of amplifier is applied as a negative feedback find out bandwidth with and without feedback, cutoff frequency and overall gain of amplifier.	<b>06</b>
2.	If $A=1000$ $\beta=10\%$ $R_i=200\Omega$ , $R_o=20K\Omega$ , $F_1=200Hz$ and $F_2=200KHz$ then find out	<b>06</b>
	1. Bandwidth without feedback.	
	2. Bandwidth With feedback.	
	3. Gain with feedback.	
	4. Input Resistance with feedback.	
	5. Output Resistance with feedback.	
	5. Cutoff Frequencies.	
	6. Output Voltage if $V_i=10mv$	
3	State the function of RFC coil.	<b>02</b>

