C.U.SHAH UNIVERSITY Summer Examination-2017

Subject Name: Electrical & Electronics Measurement

	Subject Code: 4TE04EEM1			Branch: B.Tech (Electrical)	
	Semeste Instruction	r: 4 Date: 11	/05/2017	Time: 02:00 To 05:00	Marks: 70
	(1) (2) (3) (4)	Use of Programmable cal Instructions written on ma Draw neat diagrams and f Assume suitable data if n	culator & any oth ain answer book a Tigures (if necessa eeded.	ner electronic instrument is are strictly to be obeyed. ary) at right places.	prohibited.
Q-1		Attempt the following	questions:		(14)
	a)	Wattmeter has two coils a) Wattmeter has two co c)Voltage and current c	s namely oils namely oild)Pressure and	 b)Voltage and resista resistance coil	nce coil
	b)	Basically a potentiomet a) comparing two volta c) comparing two curre	er is a device for ges b) t ntsd) none of abo	measuring a current	
	c)	For measurements on h a) Wein bridge b) Modi c) Schering bridge	igh voltage capac fied De Sauty's b d) any of abov	itors, the suitable bridge is ridge ve	3
	d)	The multiplier and the r a) series b c) series-paralleld) none	neter coil in a vol) parallel e of above	ltmeter are in	
	e)	The operating voltage of a) 6 V c) 40 V	f a meggar is abo b) 12 V d) 100 V	put	
	f)	Standard resistor is mac a) maganin b) pla c) silver d) copper	le from tinum		
	g)	Most sensitive Galvano a) elastic galvanometer c) spot ballistic galvano	meter is o) vibration galva meterd) none of a	above	
	h)	The pointer of an indica a) very light c) either A) or B)	nting instrument s b) very hea d) neither	hould be avy A) or B)	
	i)	In majority of instrumer a) fluid friction c) eddy current	nts damping is pr b) d)bo	ovided by spring oth A) and B)	
			Page 1	3	



j)	To avoid the effect	t of stray m	agnetic field in A.C. bridges we can use		
	a) magnetic screening		b) Wagner earthing device		
	c) wave filters	d) none of	of above		

- k) Define: Repeatability
- **I**) Define: Accuracy
- **m**) What is the use of De Sauty's Bridge?
- **n**) What is the unit of energy measured by energy meter?

Attempt any four questions from Q-2 to Q-8

Q-2		Attempt all questions	(14)
	(a)	Explain Maxwell's bridge for measurements of unknown inductance. Determine condition for balance.	07
	(b)	Explain the Schering bridge in details.	07
Q-3		Attempt all questions	(14)
	(a)	Explain with the help of neat diagram the working of a digital voltmeter.	07
	(b)	What is effect of change in burden & burden power factor on the ratio & phase angle of PTs?	07
Q-4		Attempt all questions	
	(a)	What are the difficulties associated with the measurement of low resistance? Describe how low resistance is measured accurately by Kelvin's double bridge.	
	(b)	Describe with the help of neat diagram the loss of charge method to determine the insulation resistance of a short length cable and derive an expression for determination of insulation resistance.	07
Q-5		Attempt all questions	
	(a)	Explain De sauty's bridge for measurements of unknown capacitance. Determine condition for balance.	07
	(b)	Which are the different A.C. bridges used for mutual inductance measurement? Explain any one in detail.	07
Q-6		Attempt all questions	(14)
	(a)	Explain Murray loop test and Varley loop test.	07
	(b)	Explain construction & working of Meggar.	07

Page 2 || 3



Q-7 Attempt all questions (14) Explain with the help of a block diagram the working of a spectrum analyzer? 07 **(a)** Where is spectrum analyzers commonly used? Explain the term "total Harmonic Distortion". Describe the functioning of a total **(b)** 07 harmonic distortion meter. Q-8 Attempt all questions (14) Draw and explain block diagram of Cathode ray oscilloscope (CRO) in brief. **(a)** 07

(b) A sheet of backellite 4.5 mm thick is tested at 50 Hz, between electrodes 0.12 m in diameter. The Schering bridge employs a standard air capacitor C₂ of 106 pF capacitance, a non-inductive resistance R_4 of $1000/\pi \Omega$ in parallel with a variable capacitor C_4 and a non-reactive resistance R₃. Balance is obtained with C₄ = 0.5 μ F & R₃=260 Ω .Calculate unknown capacitance, power factor and relative permittivity of sheet.

Page 3 || 3

