

mentioned

- 13) Schmitt trigger uses
(a) positive feedback (b) negative feedback (c) compensating capacitors (d) pull up resistors

- 14) Define: CMRR

Attempt any four questions from Q-2 to Q-8

- Q-2 Attempt all questions (14)**
(a) What is op-amp? Draw and explain the block diagram representation of a typical Op-amp. (07)
(b) Draw & Explain Constant Current source Circuit. (07)
- Q-3 Attempt all questions (14)**
(a) Define: 1) Input Bias Current 2) PSRR 3) Slew rate 4) Input offset current 5) Input offset voltage (05)
(b) Explain the open loop op-amp configuration with waveform. (05)
(c) Why op-amp is generally not used in open loop mode? (04)
- Q-4 Attempt all questions (14)**
(a) Draw and explain the Block Diagram of IC 555 Timer. (05)
(b) Explain the Block Diagram of Voltage Controlled Oscillator(566/VCO) (05)
(c) Explain Phase Shift Oscillator. (04)
- Q-5 Attempt all questions (14)**
(a) Explain the Practical Differentiator circuit. Explain its advantages. (07)
(b) Draw and Explain Differential input Differential output amplifier. (07)
- Q-6 Attempt all questions (14)**
(a) Explain the working of inverting summing amplifier. (07)
(b) Explain Basic Inverting Schmitt trigger circuit with input & output waveforms. (07)
- Q-7 Attempt all questions (14)**
(a) Compare Butterworth filter & Chebychev Filters. (07)
(b) Design a practical integrator circuit with a d.c gain of 10, to integrate a square wave of 10 KHz (07)
- Q-8 Attempt all questions (14)**
(a) Explain the Frequency Shift keying Demodulator circuit using PLL. (05)
(b) Explain the operation of Voltage to current converter with floating load. (05)
(c) Explain Window Detectors. (04)

