

- A) 40 % B) 50 % C) 75 % D) 81 %
- 8) Ripple factor of a half wave rectifier is _____
 A) 100 % B) 50 % C) 121 % D) 0 %
- 9) In an enhancement type MOSFET, channel permanently exists.
 A) True B) False
- 10) In a transistor lightly doped part is _____
 A) Base B) Collector C) Emitter D) None of the above
- 11) In a P-N-P transistor, base is made of N type material.
 A) True B) False
- 12) If the base emitter junction and base collector junction of BJT both are forward biased, BJT operates in _____ region.
 A) Active B) Cut-off C) Saturation region D) None of the above
- 13) List the characteristics of laser.
- 14) Give any two difference between stimulated emission and spontaneous emission.

Attempt any four questions from Q-2 to Q-8

- Q-2 Attempt all questions (14)**
- (a) Explain the formation of P- type semiconductors. **07**
- (b) Classify the conductors, insulators and semiconductors with the help of energy band theory. **07**
- Q-3 Attempt all questions (14)**
- (a) Draw the V-I characteristics of diode and explain how diode works in forward bias condition. **07**
- (b) Draw the symbol and V-I characteristics of zener diode and discuss various regions of the characteristics. **07**
- Q-4 Attempt all questions (14)**
- (a) Draw the circuit diagram and waveforms of full wave bridge rectifier and explain its operation. **07**
- (b) Draw the circuit diagram, input and output voltage waveforms for below circuits. **07**



- i) Series Positive Clipper Circuit
- ii) Negative Clamper Circuit

Q-5 **Attempt all questions** **(14)**

- (a) Draw the circuit of common base configuration for BJT. Draw its output characteristics and explain regions of output characteristics. **07**
- (b) A full wave rectifier circuit is fed from a transformer having a centre-tapped secondary winding. The *rms* voltage from a either end of secondary to centre tap is 30 V. If the diode forward resistance is 20 Ω and that of the half secondary is 8Ω, for a load of 1 k Ω. Calculate, **07**
 - i) Maximum value of load current
 - ii) Average value of load current
 - iii) RMS value of load current

Q-6 **Attempt all questions** **(14)**

- (a) Explain the transistor action with the help of an NPN transistor and show that $I_E = I_B + I_C$. Where I_B = Base Current, I_E = Emitter Current, I_C = Collector Current **07**
- (b) Determine the following parameters for the below network. **07**
 - i) Base Current I_B ii) Collector current I_C iii) Collector Emitter Voltage V_{CE}



