

Enrollment No: _____

Exam Seat No: _____

C.U.SHAH UNIVERSITY

Summer Examination-2018

Subject Name: Analog and Digital Electronics

Subject Code: 4SC04ADE1

Branch: B.Sc. (Chemistry, Physics)

Semester: 4

Date: 10/05/2018

Time: 10:30 To 1:30

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1	Attempt the following questions:	(14)
	a) What is Amplifier?	1
	b) Define stabilization and give formula of stabilization factor.	1
	c) Give full form of JFET.	1
	d) Define voltage gain of amplifier.	1
	e) Give full form of UJT and draw its symbol.	1
	f) What is OP-Amp?	1
	g) Define Analog signal.	1
	h) Give the name of transistor biasing method.	1
	i) What is phase reversal?	1
	j) Define Transconductance of JFET.	1
	k) Define pinch-off voltage.	1
	l) Convert $(829)_{10}$ into binary number system.	1
	m) Define Bandwidth.	1
	n) Give Barkhausen's criterion for self sustained oscillations.	1
	Attempt any four questions from Q-2 to Q-8	
Q-2	Attempt all questions	(14)
	a) Explain in details Base resistor method of transistor biasing.	5
	b) Explain in details construction and working of JFET.	5
	c) Give differences between BJT and JFET.	4
Q-3	Attempt all questions	(14)
	a) Explain in details Voltage divider method of transistor biasing.	5
	b) Explain in details construction and working of MOSFET.	5
	c) Write a short note on OR Gate in details	4
Q-4	Attempt all questions	(14)
	a) Explain in details construction and working of UJT.	6
	b) Explain any two applications of OP-Amp.	6
	c) What Is Thermistor?	2



Q-5	Attempt all questions	(14)
	a) Explain in details AND gate with two inputs logic diagram and its truth table.	5
	b) Explain in details parameters of JFET.	6
	c) Give classification of amplifier.	3
Q-6	Attempt all questions	(14)
	a) Explain in details Barkhusen's criterion for self sustained oscillations in details.	5
	b) Give characteristics of Ideal Op-Amp.	5
	c) Simplify the following Boolean expression: $Y = (A+B+C) \cdot (A+B)$	4
Q-7	Attempt all questions	(14)
	a) Explain in details NAND Gate as a universal gate.	6
	b) Explain in details Half adder and full adder circuits.	6
	c) Explain Binary addition with examples.	2
Q-8	Attempt all questions	(14)
	a) Explain in details practical circuit of transistor amplifier.	5
	b) Explain in details NOT Gate with its logic circuit diagram.	5
	c) State and prove any two De Morgan's theorems.	4

