

Enrollment No: _____

Exam Seat No: _____

C.U.SHAH UNIVERSITY

Summer Examination-2018

Subject Name: Solid State Electronics

Subject Code: 4SC06SEC1

Branch: B.Sc. (Physics)

Semester: 6

Date: 04/05/2018

Time: 2:30 To 5:30

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1	Attempt the following questions:	(14)
	a) Define Multivibrator.	1
	b) Give the types of Switch.	1
	c) Give one application of SCR.	1
	d) What is Clamper?	1
	e) What is OP-AMP?	1
	f) Give types of modulation.	1
	g) Define Bandwidth.	1
	h) Give types of communication systems.	1
	i) Give application of clipper circuits.	1
	j) Give full form of SCR.	1
	k) Define latching current of Thyristors.	1
	l) What is clipping?	1
	m) Give types of Multivibrators.	1
	n) Define frequency modulation.	1
	Attempt any four questions from Q-2 to Q-8	
Q-2	Attempt all questions	(14)
	a) Explain in details Switching action of a Transistor.	5
	b) Explain principle of operation of an SCR with diagram in details.	5
	c) Explain in details Differentiating circuit.	4
Q-3	Attempt all questions	(14)
	a) Explain in details Transistor Bistable Multivibrator.	6
	b) Explain in details output characteristics of SCR with figure.	4
	c) Explain Integrating circuit in details.	4
Q-4	Attempt all questions	(14)
	a) Explain in details Transistor Astable Multivibrator.	6
	b) Write a short note on TRIAC in detail.	5
	c) Write a short note on Clamper circuit.	3



Q-5	Attempt all questions	(14)
	a) Explain in detail Diode clipping circuits with diagram.	7
	b) Explain in detail modulation index and percentage of modulation.	7
Q-6	Attempt all questions	(14)
	a) Explain elements of a communication system in detail.	5
	b) Write a short note on DIAC.	5
	c) Explain in detail any two triggering methods of a Thyristors.	4
Q-7	Attempt all questions	(14)
	a) Explain in detail two transistor analogy of SCR.	5
	b) Explain in detail any two applications of OP-AMP.	6
	c) Give classification of ICs on scale of integration.	3
Q-8	Attempt all questions	(14)
	a) Explain in detail How Monolithic ICs are made?	6
	b) Explain in detail principle of amplitude modulation.	5
	c) Give advantages of ICs in detail.	3

