

C.U.SHAH UNIVERSITY

Summer Examination-2018

Subject Name: Electrical & Electronics Measurement

Subject Code: 4TE04EEM1

Branch: B.Tech (Electrical)

Semester: 4

Date: 03/05/2018

Time: 10:30 To 01:30

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1 Attempt the following questions:

(14)

- a) Megger is used to measure _____ (Fill the blank).
- b) Cable is generally made up of _____
a) copper b) Aluminum c) wood d) None of the above
- c) In an Anderson bridge, the unknown inductance is measured in terms of
a) known inductance and resistance b) known Capacitance and resistance c) known resistance d) none of the above
- d) True value of resistance is equal to the measured value only if the resistance of voltmeter is infinite. True or false
- e) A moving iron instrument can be used for
(a) D.C. only (b) A.C. only (c) Both A.C. & D.C. (d) None of above
- f) Frequency can be measured by using
(a) Maxwell's bridge (b) Schering bridge
(c) Heaviside Campbell bridge (d) Wien's bridge.
- g) The material of wires used for making resistance standards is usually:
(a) manganin (b) nichrome (c) copper (d) phosphor Bronze
- h) An induction meter can handle current up to____
a) 30 A b) 60 A c)50A d)100A
- i) An 0-10 A ammeter has a guaranteed accuracy of 1 percent of full scale deflection. The limiting error while reading 2.5 A is
a)1 % b) 2% c) 4% d) None of the above
- j) The use of _____ instruments is merely confined within laboratories as standardizing Instruments.
(a) indicating (b) absolute (c) recording (d) integrating
- k) Wattmeter has two coils namely _____
(a) voltage and pressure coil (b) voltage and resistance coil
(c) voltage and current coil (d) pressure and resistance coil
- l) Maxwell's inductance-capacitance bridge is used for measurement of inductance of
(a) Low Q coils (b) medium Q coils (c) high Q coils (d) Low& medium Q coils
- m) The unit of Ammeter Sensitivity is



- a)volt b) ohm c)Volt/ohm d)ohm/volt
- n) A 0-300V voltmeter has an error of $\pm 2\%$ of full scale deflection. What would be the range of reading if true voltage is 30V?
 a)24V-36V b)29.4V -30.6V c)20V -40V d)none of the above

Attempt any four questions from Q-2 to Q-8

- Q-2 Attempt all questions (14)**
 (a) Explain different types of errors that may occur in measurements.
 (b) What are the different methods to measure high resistance? Explain any one in detail.
- Q-3 Attempt all questions (14)**
 (a) Explain De Sauty's bridge with Phasor diagram.
 (b) What are the difficulties associated with the measurement of low resistance? Describe how low resistance is measured accurately by Kelvin's double bridge.
- Q-4 Attempt all questions (14)**
 (a) Explain Hay's bridge with advantages and disadvantages.
 (b) Define the terms: (1) Accuracy (2) Precision (3) Resolution (4) Sensitivity (5) Reproducibility (6) Error (7) Drift
- Q-5 Attempt all questions (14)**
 (a) Write a short note on spectrum analyzer.
 (b) Explain working principle of induction type energy meter.
- Q-6 Attempt all questions (14)**
 (a) Explain construction & working of Meggar.
 (b) Explain construction and working of current transformer with the help of phasor diagram.
- Q-7 Attempt all questions (14)**
 (a) Explain the principle and operation of Potential Transformer and also discuss the Ratio and Phase angle error.
 (b) Write short note on flux meter.
- Q-8 Attempt all questions (14)**
 (a) A sheet of backellite 4.5 mm thick is tested at 50 Hz, between electrodes 0.12 m in diameter. The Schering bridge employs a standard air capacitor C_2 of 100 pF capacitance, a non-inductive resistance of $1000/\pi \Omega$ in parallel with a variable resistance R_3 . Balance is obtained with $C_4 = 0.5 \mu\text{F}$ & $R_3 = 260 \Omega$. Calculate unknown capacitance, power factor and relative permittivity of sheet.
 (b) A CRT has an anode voltage of 2000V and parallel deflecting plates 2 cm long and 5 mm apart. The screen is 30 cm from the centre of the plates. find the input voltage required to deflect the beam through 3 cm. The input voltage is applied to the deflecting plates through amplifiers having an overall gain of 100.

