

Enrollment No: _____

Exam Seat No: _____

C.U.SHAH UNIVERSITY

Summer Examination-2018

Subject Name : Digital Electronics and Digital Instruments

Subject Code : 2TE04DEI1

Branch: Diploma (Electrical)

Semester : 4

Date : 05/05/2018

Time : 10:30 To 01:30

Marks : 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
- (2) Instructions written on main answer book are strictly to be obeyed.
- (3) Draw neat diagrams and figures (if necessary) at right places.
- (4) Assume suitable data if needed.

Q-1

Attempt the following questions:

(14)

- a) $A+A = \underline{\hspace{2cm}}$
1. 0
 2. 1
 3. A
 4. A^2
- b) If $A = 01001$, $A'' =$
1. 10111
 2. 01001
 3. 11011
 4. 10110
- c) How many Inputs does full adder has?
1. 1
 2. 2
 3. 3
 4. 4
- d) The number of digits in Octadecimal system are:-
1. 10
 2. 15
 3. 16
 4. 8
- e) Full form of POS is:-
1. Some of Parts
 2. Sum of Product
 3. Some of Product
 4. Sum of power
- f) Which Gate works as Universal Gate?
- | | |
|-----------|---------|
| 1. EX-OR | 3. NAND |
| 2. EX-NOR | 4. OR |
- g) $(101)_2 + (011)_2 = (\underline{\hspace{2cm}})_2$



1. 1000
 2. 101
 3. 1010
 4. 112
- h) A small circle on the output of a logic gate is used to represent the:
1. Comparator operation.
 2. OR operation.
 3. NOT operation.
 4. AND operation.
- i) The format used to present the logic output for the various combinations of logic inputs to a gate is called a(n):
1. Truth table.
 2. Input logic function.
 3. Boolean constant.
 4. Boolean variable.
- j) Which of the examples below expresses the distributive law?
1. $(A + B) + C = A + (B + C)$
 2. $A(B + C) = AB + AC$
 3. $A + (B + C) = AB + AC$
 4. $A(BC) = (AB) + C$
- k) Which of the following is a form of De Morgan's Theorem?
1. $\overline{X + Y} = \overline{X} + \overline{Y}$
 2. $X(1) = X$
 3. $\overline{XY} = \overline{X} + \overline{Y}$
 4. $X + 0 = 0$
- l) Which of the following expressions is in the sum-of-products (SOP) form?
1. $(A + B)(C + D)$
 2. $(A)B(CD)$
 3. $AB(CD)$
 4. $AB + CD$
- m) Applying DeMorgan's theorem to the expression \overline{ABC} , we get _____.
1. $\overline{A + B + C}$
 2. $\overline{A} + \overline{B} + \overline{C}$
 3. $A + \overline{B} + C\overline{C}$
 4. $A(B + C)$
- n) The systematic reduction of logic circuits is accomplished by:
1. using Boolean algebra
 2. symbolic reduction
 3. TTL logic
 4. using a truth table.

Attempt any four questions from Q-2 to Q-8

Q-2

Attempt all questions

(14)

A Solve the following:

(2)



1. $(11011011)_2 + (0101101)_2$ (2)
2. $(1101.110)_2 - (100.011)_2$ (3)
3. $(11001.101)_2 * (11.101)_2$
- B** Explain NAND & NOR Gates with Figures and Truth Tables. (7)
- Q-3** **Attempt all questions** (14)
- A** Write De-Morgan's Theorem. Explain with the help of neat and clean figure. (7)
- B** Find SOP:- (7)
- $Y = f(A, B, C, D) = ABCC + ABB + AAC$
- Find POS:-
- $Y = f(A, B, C, D) = (A+BB)(A+CC)(A+BB+D)$
- Q-4** **Attempt all questions** (14)
- A** Draw and Explain Block Diagram of D/A Converter. Give types of D/A Converter. (7)
- B** Explain BCD to Seven Segment Decoder. (7)
- Q-5** **Attempt all questions** (14)
- A** Draw the logic diagrams for the following:- (7)
- i. $Y = AB+AB+BC$
- ii. $Y = ABC+ABD+AC$
- iii. $Y = (A+B)(A+C)(A+B+D)$
- B** Write the types of A/D Converter. Explain any one A/D Converter with neat and clean figure. (7)
- Q-6** **Attempt all questions** (14)
- A** What is Encoder? Explain Octal to Binary encoder. (7)
- B** What is Flip-Flop? Explain R-S Flip Flop with block diagram, logic diagram and truth table. (7)
- Q-7** **Attempt all questions** (14)
- A** Explain Basic Building Blocks Of Digital Instruments. (7)
- B** Explain half adder with the help of necessary diagram. (7)
- Q-8** **Attempt all questions** (14)
- A** Explain J-K And Master Slave J-K Flip Flop. (7)
- B** Explain Watt Meter. (7)







