

(a) they are equal value (b) they are connected in parallel (c) they are equal (d) They are unequal

n) Obtain the Laplace Transform for $f_1(t) = t$

Attempt any four questions from Q-2 to Q-8

Q-2 Attempt all questions (14)

(a) Explain the poles and zeros of the network function. State its important features. (07)

(b) Write down voltage and current relationships in resistor, inductor and capacitor. (07)
Obtain these relationships in “s” domain also. State assumptions if any in obtaining the relationship.

Q-3 Attempt all questions (14)

(a) Use nodal analysis to find the voltage across the 5Ω resistor in the network of Fig.1 (07)

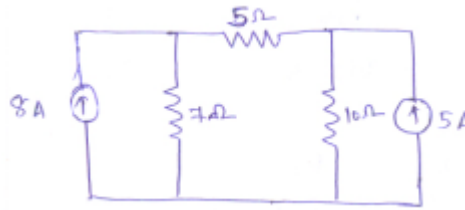


Fig.1

(b) Find the currents I_1 , I_2 and I_3 in the given network of Fig 2 using mesh analysis. (07)

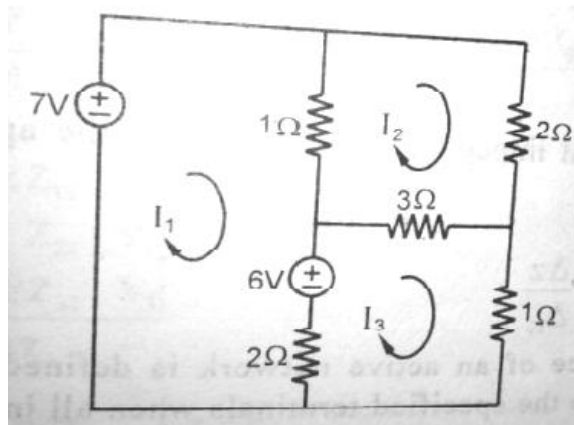


Fig.2

Q-4 Attempt all questions (14)

(a) Explain following terms of graph in network terminology with suitable example. (05)

(i) Tree (ii) Twing (iii) Link (iv) Co-tree (v) Incidence Matrix

(b) Explain Ideal and Practical Energy sources. (05)

(c) Write a note on coefficient of coupling. (04)

Q-5 Attempt all questions (14)

(a) State maximum power transfer theorem and obtain proof of maximum power transfer theorem. (05)

(b) Explain Laplace transform of Exponential Function. (05)

(c) State and explain Kirchoff's Laws with a suitable example. (04)

Q-6 Attempt all questions (14)

(a) Explain source transformation. (05)

(b) Find the voltage across $1\text{ k}\Omega$ resistor in the circuit shown in Fig.3 using superposition (05)



theorem.

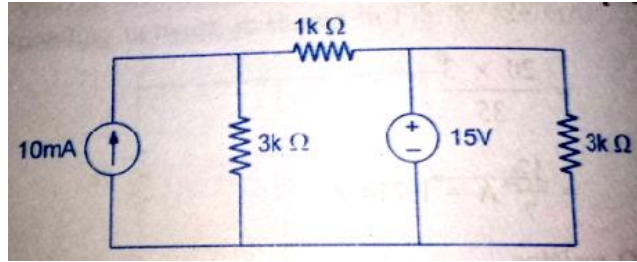


Fig.3

- (c) The Z-Parameters of a circuit are given by $\begin{bmatrix} 4 & 1 \\ 3 & 3 \end{bmatrix}$ Find the transmission parameters. (04)

Q-7 Attempt all questions (14)

- (a) Find the relation between ABCD parameter and Z- parameter & also find Vice-Versa. (07)

- (b) A series R-L circuit is in parallel with a capacitance. Find the input impedance in Laplace domain. (07)

Q-8 Attempt all questions (14)

- (a) In the network of Fig.4 the switch K is moved from 1 to 2 position at $t=0$, steady state having previously been attained. Find the current $V_c(t)$. (07)

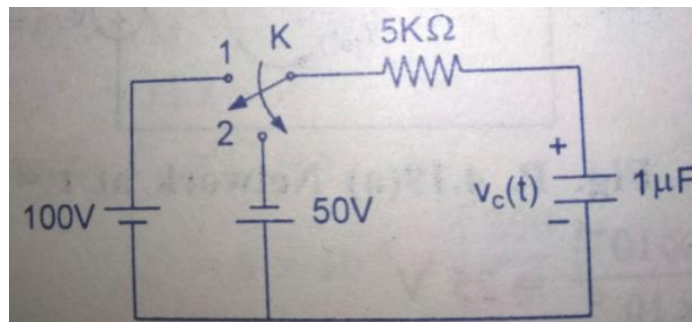


Fig.4

- (b) In the network of the Fig.5 the switch k is closed at $t=0$ with the capacitor uncharged and with zero current in the inductor. Find the values of i , di/dt and d^2i/dt^2 at $t=0^+$. if $V=100V$, $R=10\Omega$, $L=1H$ and $C=10\mu F$. (07)

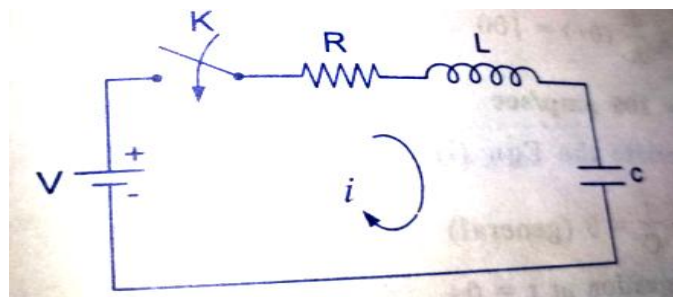


Fig.5

