

Enrollment No: _____

Exam Seat No: _____

C.U.SHAH UNIVERSITY

Winter Examination-2018

Subject Name: Analog and Digital Electronics

Subject Code: 4SC04ADE1

Branch: B.Sc. (Chemistry, Physics)

Semester: 4

Date: 08/10/2018

Time: 10:30 To 1:30

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1	Attempt the following questions:	(14)
	a) Give full form of MOSFET and draw its symbol.	1
	b) What do you mean by stabilization in a transistor?	1
	c) What is CMRR in Op-Amp operation?	1
	d) Define voltage gain of an amplifier.	1
	e) Give the working of an Amplifier	1
	f) What is Op-Amp?	1
	g) Give Barkhausen's criterion for self-sustained oscillations.	1
	h) What is the value of input resistance for an ideal Op-Amp circuit?	1
	i) List the names of the basic logic gates.	1
	j) What is phase reversal?	1
	k) Differentiate between Analog and Digital signals.	1
	l) Define pinch-off voltage.	1
	m) Convert $(10101)_2$ into decimal number.	1
	n) Give two applications of Op-Amp	1

Attempt any four questions from Q-2 to Q-8

Q-2	Attempt all questions	(14)
	a) Explain voltage divider bias method of transistor biasing.	5
	b) Explain in detail construction and working of JFET.	5
	c) Explain in detail OR Gate with its logic diagram and truth table.	4
Q-3	Attempt all questions	(14)
	a) Enumerate on Base resistor method of transistor biasing.	5
	b) Write a note on UJT.	5
	c) Enlist the main differences between BJT and JFET.	4
Q-4	Attempt all questions	(14)
	a) Explain in detail AND gate with two inputs logic diagram and its truth table.	6
	b) Explain two applications of Op-Amp.	6
	c) Give an account on Binary addition with examples.	2



Q-5	Attempt all questions	(14)
	a) Give the technical characteristics of an Ideal Op-Amp with their values..	5
	b) Explain in detail parameters of JFET.	6
	c) Give the classifications of amplifier	3
Q-6	Attempt all questions	(14)
	a) Explain in details Barkhausen's criterion for self-sustained oscillations.	5
	b) Explain the practical circuit of transistor amplifier in detail	5
	c) Explain the construction of MOSFET with diagram.	4
Q-7	Attempt all questions	(14)
	a) Explain in detail NAND Gate as a universal gate.	6
	b) Write a note on NOT Gate with its logic circuit diagram.	5
	c) Give the function and working of a thermistor	3
Q-8	Attempt all questions	(14)
	a) Explain in detail Half adder and Full adder circuits.	5
	b) State and prove De Morgan's theorem.	6
	c) Simplify the following Boolean expression:	3
	$Y = AB + ABC + ABC$	

