

**C.U.SHAH UNIVERSITY**  
**Winter Examination-2018**

**Subject Name: Linear Electronics**

**Subject Code: 4TE03LNE1**

**Branch: B.Tech (CE)**

**Semester: 3**

**Date: 01/12/2018**

**Time: 02:30 To 05:30**

**Marks :70**

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
- (2) Instructions written on main answer book are strictly to be obeyed.
- (3) Draw neat diagrams and figures (if necessary) at right places.
- (4) Assume suitable data if needed.

---

**Q-1**                      **Attempt the following questions:** **(14)**

- a) What is the use of class C amplifiers?
- b) Why a power amplifier is called large signal amplifier?
- c) What are the practical application of emitter follower?
- d) Define Cross Over Distortion.
- e) Define Oscillator.
- f) Define Q Point of transistor.
- g) What do you understand by feedback in an amplifiers?
- h) Why do we use transformer in the output stage of power amplifier?
- i) Give the difference between voltage and power amplifier.
- j) Define Barkhausen Criterion for Feedback Oscillator.
- k) Define Positive Feedback.
- l) Define CMRR.
- m) Define Slew Rate.
- n) Why an emitter follower is called so?

**Attempt any four questions from Q-2 to Q-8**

**Q-2**                      **Attempt all questions** **(14)**

- (a) Explain h-parameter analysis of CE amplifier
- (b) Define two port devices. Explain transistor hybrid model in detail.

**Q-3**                      **Attempt all questions** **(14)**

- (a) Write a note on Emitter Follower in detail.
- (b) Explain the working of Class B transformer coupled push-pull amplifier and derive the expression for its efficiency.

**Q-4**                      **Attempt all questions** **(14)**

- (a) What is biasing? State the need of it. Explain fixed bias in detail.
- (b) What is operating point? State the importance of it. Explain any one method for maintain it in active region with necessary figure.



- Q-5** **Attempt all questions** (14)
- (a) Explain working Colpitt's Oscillator with help of circuit diagram.
  - (b) Explain Crystal oscillator in detail.
- Q-6** **Attempt all questions** (14)
- (a) Show that maximum collector efficiency of class A transformer coupled power amplifier is 50%.
  - (b) Draw and explain Current Series Feedback Amplifier in detail.
- Q-7** **Attempt all questions** (14)
- (a) Draw the block diagram of basic op-amp and explain the function of each block in detail.
  - (b) Derive an expression for the voltage gain of a Non-Inverting Op-Amp.
- Q-8** **Attempt all questions** (14)
- (a) Explain summing amplifier using inverting configuration.
  - (b) Write short note on Hartley's Oscillator.

