

**C.U.SHAH UNIVERSITY**  
**Winter Examination-2018**

**Subject Name : Circuit Theory**

**Subject Code : 4TE03CIT1**

**Branch: B.Tech (EEE, Electrical)**

**Semester : 3**

**Date : 04/12/2018**

**Time : 02:30 To 05:30**

**Marks : 70**

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
  - (2) Instructions written on main answer book are strictly to be obeyed.
  - (3) Draw neat diagrams and figures (if necessary) at right places.
  - (4) Assume suitable data if needed.
- 

**Q-1 Attempt the following questions: (14)**

- a)  $V = I * \underline{\hspace{2cm}}$  (R, L, C) . Fill the best option using ohm's Law.
- b) Battery is an example of \_\_\_\_\_( Voltage source, Current Source)
- c) Draw the symbol of an ideal voltage source.
- d)  $V = V_1 + V_2 + V_3$  . This formulae is applicable to series circuit.(True/False)
- e) State the name of sources applicable to circuit operation.
- f) State the name of analytical methods using which the network can be simplified.
- g) State the name of any two network theorem applicable to circuit solution.
- h) What is linear differential equation? Give suitable example.
- i) State what do you mean by open circuit and short circuit ?
- j) The Laplace transform of  $f(t) = 1/t$  is \_\_\_\_\_ (1,  $1/s^2$ , 0, -1)
- k) The inverse Laplace Transform of  $(1/s)$  is \_\_\_\_\_. (1, 0,  $t^2$ , sint)
- l) The poles of the transfer function is a value where function is infinite.(True/False)
- m) Write down the equation of two port network in terms of ABCD parameters.
- n) Draw the circuit of Lattice network.

**Attempt any four questions from Q-2 to Q-8**

**Q-2 Attempt all questions (14)**

- (a) State and explain Kirchoff's Current Law and Voltage Law. (7)
- (b) Find the value of total current and equivalent resistance when two resistors (7)  
having value of 6 ohm and 4 ohm are connected in (i) series combination (ii)  
parallel combination . The source voltage is 10 V.

**Q-3 Attempt all questions (14)**


- (a) Briefly explain about ideal current sources and ideal voltage sources. (7)
- (b) Briefly explain about graph and its subparts with suitable example. (7)

**Q-4 Attempt all questions (14)**

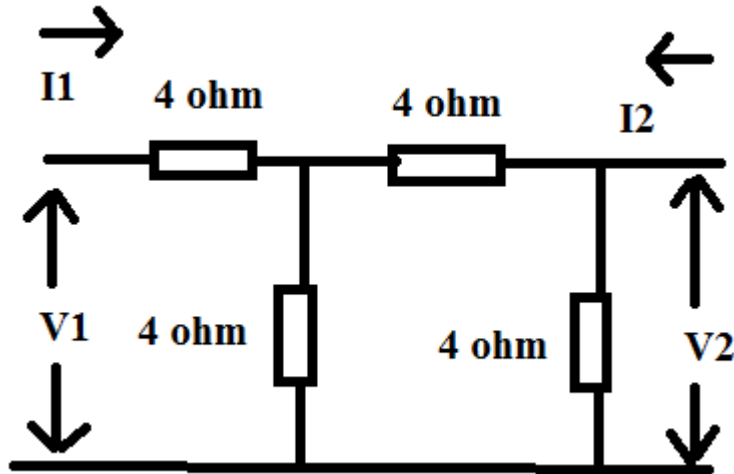- (a) Explain Thevenin's Theorem. (7)
- (b) State the Super Position Theorem with suitable examples. (7)




- Q-5** **Attempt all questions** (14)
- (a) Write down voltage and current relationships in resistor, inductor and capacitor. (7)  
Obtain these relationships in “s” domain also. State assumptions if any in obtaining the relationship.
- (b) For the network shown in the figure find the value of h parameters. (7)



- Q-6** (14)
- The open circuit impedance parameters of a two port network are  $Z_{11}=5\Omega$ ,  $Z_{22}=4\Omega$ ,  $Z_{12}=Z_{21}=3\Omega$ . Find the ABCD parameter of the network.

- Q-7** **Attempt all questions** (14)
- (a) Find the Laplace transformation of  $\sin(t)$ ,  $e^{at}$ . (7)
- (b) Find the inverser Laplace Transformation of  $(s/s^2+a^2)$  (7)

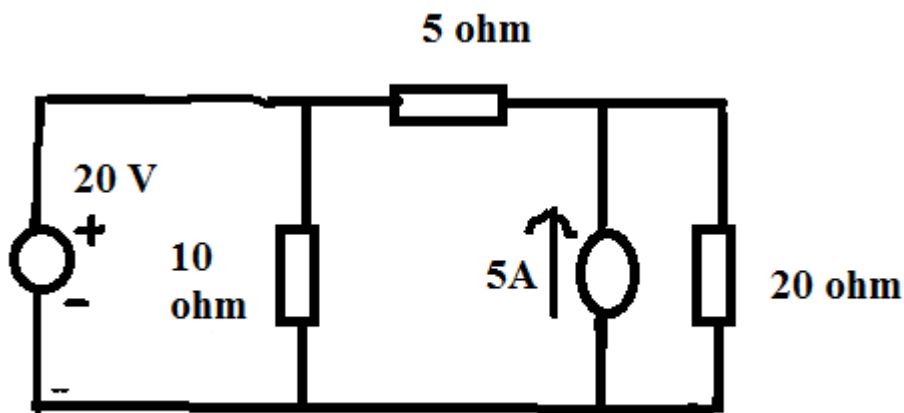- Q-8** **Attempt all questions** (14)
- (a) Find the power loss across the 5 ohm resistor. (7)



- (b) Explain the terms ( i ) Non-Linear (ii) Uni-lateral ( iii) Passive (iv) Reciprocal (7)  
(v) Time variant (vi) Lumped parameter and (vii) Dual with reference to Network

