

C.U.SHAH UNIVERSITY

Winter Examination-2018

Subject Name: Digital Circuits

Subject Code: 4TE03DCI1

Branch: B.Tech (Electrical)

Semester: 3

Date: 01/12/2018

Time: 02:30 To 05:30

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1 Attempt the following questions: (14)

- 1) The bit 0 and 1 represents _____ number system.
A) Binary B) Octal C) Hexadecimal D) Decimal
- 2) The NOT gate represents the opposite output status of input signal.
A) True B) False
- 3) The Number F represents _____ number in hexadecimal system.
A) 11 B) 10 C) 14 D) 15
- 4) The binary equivalent of 4 is _____.
A) 001 B) 100 C) 101 D) 000
- 5) NOR gate is used as universal Gate.
A) True B) False
- 6) The Decimal number systems have _____ digits.
A) 0 to 1 B) 0 to 9 C) 0 to F D) None of the above
- 7) Which type of logic gate is also defined as an inverter?
A) OR Gate B) NOR Gate C) NOT Gate D) NAND Gate
- 8) In the positive logic system 1 is high and 0 is low.
A) True B) False
- 9) Any basic gate can be used in combinational logic circuit.
A) True B) False
- 10) The binary system is based on the principle of _____.
A) Boolean Algebra B) Ordinary Algebra C) Complex Algebra



D) Any of the above

- 11) An n variable K-map have _____ cells
A) n^2 B) 2^n C) n^n D) n^{2n}
- 12) A flip flop has two outputs which are _____
A) Always 0 B) Always 1 C) Always Complementary D) None of the above
- 13) Write the full form of BCD?
- 14) Draw the symbol of exclusive OR gate (XOR) and exclusive NOR gate (X-NOR).

Attempt any four questions from Q-2 to Q-8

- Q-2 Attempt all questions (14)**
- (a) Simplify the below shown expression. **07**
- i) $x + x'y = x + y$ ii) $x(x'+y) = xy$
- (b) Do as directed. **07**
- i) Convert $(10101)_2$ to decimal.
- ii) Convert $(52)_{10}$ to binary.
- iii) Write the 1's complement of 01001001.
- iv) Convert the decimal number $(378)_{10}$ to octal.
-
- Q-3 Attempt all questions (14)**
- (a) Explain any four laws of Boolean algebra. **07**
- (b) Explain the BCD system briefly. **07**
-
- Q-4 Attempt all questions (14)**
- (a) Draw the symbol of AND GATE and NAND GATE. Write its truth table and boolean expression. **07**
- (b) Draw the symbol of OR GATE and NOR GATE. Write its truth table and boolean expression. **07**
-
- Q-5 Attempt all questions (14)**
- (a) Convert the below expression to min terms. **07**
- i) $\bar{A} + \bar{B}\bar{C}$ ii) $\bar{A} + B + CA$
- (b) Convert the below expression to max terms. **07**
- i) $A(B + \bar{C})$ ii) $(A + \bar{B})(\bar{A} + D)$
-
- Q-6 Attempt all questions (14)**
- (a) Draw the logic diagram and truth table of HALF ADDER. Write its Boolean **07**



expression and explain its operation.

- (b) Draw the logic diagram and truth table of HALF SUBTRACTOR. Write its Boolean expression and explain its operation. **07**

Q-7 Attempt all questions (14)

- (a) Draw the logic diagram and truth table of S-R latch and explain its operation. **07**
(b) Draw the logic diagram and truth table of J-K flip-flop and explain its operation. **07**

Q-8 Attempt all questions (14)

- (a) Draw the logic diagram of 4-bit buffer register and explain its operation. **07**
(b) Draw the logic diagram and truth table 1-bit magnitude comparator and explain its operation. **07**

