



|            |  |             |
|------------|--|-------------|
| <b>Q-3</b> | <b>Attempt all questions</b>   | <b>(14)</b> |
|            | (a) Derive the equations for T to $\pi$ and $\pi$ to T network transformation.   | <b>07</b>   |
|            | (b) State and prove Maximum transfer theorem.  | <b>07</b>   |
| <b>Q-4</b> | <b>Attempt all questions</b>   | <b>(14)</b> |
|            | (a) State and prove Norton's theorem.  | <b>06</b>   |
|            | (b) Explain in detail with examples KCL and KVL laws.  | <b>05</b>   |
|            | (c) Define the terms: 1. Mesh 2. Node 3. Branch.   | <b>03</b>   |
| <b>Q-5</b> | <b>Attempt all questions</b>   | <b>(14)</b> |
|            | (a) What do you mean resonance w.r.to RLC series circuit? Obtain the expression of resonance frequency in series RLC circuit. Derive the relation between Q-factor and bandwidth in series RLC circuit.                | <b>07</b>   |
|            | (b) An RLC series circuit with resistance of $25\Omega$ is required to resonate at 100 Hz. The bandwidth is required to be 60 Hz. Determine the values of L, C, Q-factor, upper cut-off and lower cut-off frequencies. | <b>07</b>   |
| <b>Q-6</b> | <b>Attempt all questions</b>   | <b>(14)</b> |
|            | (a) Explain single and double tuned air core transformer used in tuned circuits with the help of necessary derivation. State one the application of them.  | <b>09</b>   |
|            | (b) Derive the equation for characteristic impedance of T-network in terms of $Z_{oc}$ and $Z_{sc}$ .  | <b>05</b>   |
| <b>Q-7</b> | <b>Attempt all questions</b>   | <b>(14)</b> |
|            | (a) Explain in detail symmetrical $\pi$ -type attenuator with necessary derivations.   | <b>06</b>   |
|            | (b) A symmetrical $\pi$ -type attenuator has series arm resistance of $300\ \Omega$ and shunt arm resistance of $500\Omega$ . Determine the characteristic impedance and attenuation.                                  | <b>08</b>   |
| <b>Q-8</b> | <b>Attempt all questions</b>   | <b>(14)</b> |
|            | (a) Where equalizer is connected in network? Draw the chart for classification of equalizers and explain in detail series equalizer with derivation of equations.  | <b>07</b>   |
|            | (b) Classify the filters on various bases. Which characteristics are possessed by an ideal filter? Explain in brief with diagram various filters which classify on the basis of frequency characteristics.             | <b>07</b>   |





- Q-4** **Attempt all questions** (14)
- (a) નોરટોન્સ થીયરમ કહો અને સાબિત કરો. 06
- (b) KCL અને KVL નિયમો દાખલાઓ સાથે સમજાવો. 05
- (c) વ્યાખ્યાયિત કરો ૧. મેષ ૨. નોડ ૩. બ્રાન્ચ. 03
- Q-5** **Attempt all questions** (14)
- (a) RLC શ્રેણી સર્કિટનાં સંદર્ભમાં રેઝોનન્સ શું છે? RLC શ્રેણી સર્કિટનું રેઝોનન્સ ફ્રિક્વન્સીનું સમીકરણ મેળવો. RLC શ્રેણી સર્કિટમાં Q-ફેક્ટર અને બેન્ડવિડ્થ વચ્ચેનો સંબંધ પ્રસ્થાપિત કરો. 07
- (b)  $25\Omega$  નાં રેજિસ્ટન્સ સાથે એક RLC શ્રેણી સર્કિટ  $100\text{Hz}$  પર રેઝોનેટ કરવાની જરૂર છે. બેન્ડવિડ્થ  $60\text{Hz}$  ની જરૂર છે. L, C, Q-ફેક્ટર, Lower Cut-off અને Higher Cut-off ફ્રિક્વન્સીનાં મૂલ્યો શોધો. 07
- Q-6** **Attempt all questions** (14)
- (a) જરૂરી ડેરિવેશનની મદદથી ટ્યુનવાળા સર્કિટ્સમાં વપરાતા સિંગલ અને ડબલ ટ્યુન્ડ એર કોર ટ્રાન્સફોર્મરને સમજાવો. તેઓની ગમે તે એક ઉપયોગિતા કહો. 09
- (b)  $Z_{oc}$  અને  $Z_{sc}$  નાં સંદર્ભમાં T-નેટવર્કના લાક્ષણિક ઈમ્પીડન્સ માટેના સમીકરણને મેળવો. 05
- Q-7** **Attempt all questions** (14)
- (a) જરૂરી ડેરિવેશનની મદદથી  $\pi$ -પ્રકારનું એટેન્યુએટર વિસ્તારપૂર્વક સમજાવો. 06
- (b) એક  $\pi$ -પ્રકારનાં એટેન્યુએટરને  $300\Omega$  નો શ્રેણી રેજિસ્ટન્સ અને  $400\Omega$  નો સમાંતર રેજિસ્ટન્સ છે. લાક્ષણિક ઈમ્પીડન્સ અને એટેન્યુએસન્સ મેળવો. 08
- Q-8** **Attempt all questions** (14)
- (a) નેટવર્કમાં ઇક્વાલાઈઝરને ક્યાં જોડવામાં આવે છે? ઇક્વાલાઈઝરનાં વર્ગીકરણનો ચાર્ટ દોરો અને શ્રેણી ઇક્વાલાઈઝરને સમીકરણો મેળવીને વિસ્તારપૂર્વક સમજાવો. 07
- (b) ફિલ્ટરને જુદાં જુદાં આધારો વડે વર્ગીકૃત કરો. આદર્શ ફિલ્ટર પાસે કઈ લાક્ષણિકતાઓ છે? ફ્રિક્વન્સી લાક્ષણિકતાનાં આધારે વર્ગીકૃત કરેલ જુદાં જુદાં ફિલ્ટરને ડાયગ્રામ સાથે ટુંકમાં સમજાવો. 07

