

C.U.SHAH UNIVERSITY

Winter Examination-2018

Subject Name: Analog and Digital Electronics

Subject Code: 5SC01ADE1

Branch: M.Sc. (Physics)

Semester: 1

Date: 03/12/2018

Time: 2:30 To 5:30

Marks: 70

Instructions:

- (1) Use of Programmable calculator and any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

SECTION – I

- Q-1** **Attempt the Following questions** **(07)**
- a. Define reverse recovery time. **02**
 - b. What is an OP-AMP? **01**
 - c. Give the full form of LDR. **01**
 - d. State the basic principle of light emitting diode. **01**
 - e. Define CMRR. **01**
 - f. What is slew rate? **01**
- Q-2** **Attempt all questions** **(14)**
- a. Explain with a proper diagram the principle, construction and working of a Light Emitting Diode. **07**
 - b. Justify the use of diode as a clipper. **07**
- OR**
- Q-2** **Attempt all questions** **(14)**
- a. Discuss the use of OP-AMP as a comparator and an inverter. **09**
 - b. Explain in detail a Monostable Multivibrator with proper circuit diagram. **05**
- Q-3** **Attempt all questions** **(14)**
- a. Briefly describe the construction, working and applications of a Photo diode. **06**
 - b. Write a note on Schmitt trigger using op-Amp. **05**
 - c. Explain in detail the use of diode as a switch. **03**
- OR**
- Q-3** **Attempt all questions** **(14)**
- a. Elaborate the construction, working and applications of a Light Dependent Resistor. **07**
 - b. Write a short note on Photo transistor. **07**



SECTION – II

- Q-4** **Attempt the Following questions** **(07)**
- a. Define Shift Register. **02**
 - b. What is a De-multiplexer? **02**
 - c. What are Encoders? **01**
 - d. Give the logic circuit of S-R-latch flip flop. **01**
 - e. Define Audio power Amplifier. **01**
- Q-5** **Attempt all questions** **(14)**
- a. What do you understand by a Multiplexer? **06**
Briefly explain a basic 2-input multiplexer with its logic diagram and truth table.
 - b. Describe a class-B push-pull power amplifier with proper circuit diagram also mention its advantages and disadvantages. **05**
 - c. Differentiate between Voltage and Power Amplifiers **03**
- OR**
- Q-5** **Attempt all questions** **(14)**
- a. Write a brief note on D-flip flop. **05**
 - b. Explain the working of Half adder with proper logic, circuit diagram and truth table. **06**
 - c. Draw the logic diagram of MASTER-SLAVE JK flip flop. **03**
- Q-6** **Attempt all questions** **(14)**
- a. Elaborate with proper circuit diagram the working of a class-A push-pull power amplifier. Mention its advantages and disadvantages. **07**
 - b. Explain along with logic diagram and truth table: **07**
 - i)BCD-Decimal Decoder
 - ii) 2-line to 4-line decoder using NAND Gates.
- OR**
- Q-6** **Attempt all Questions** **(14)**
- a. Explain in detail Shift register mode of Serial input - Serial output with its logic diagram. **07**
 - b. Describe the working of S-R latch flip flop using NAND Gates. Mention its truth table also. **05**
 - c. Define RAM. **02**

