

C.U.SHAH UNIVERSITY

Summer Examination-2019

Subject Name: Circuit Theory

Subject Code: 4TE03CIT1

Branch: B.Tech (Electrical)

Semester: 3 Date: 18/03/2019

Time: 2:30 To 5:30

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1 Attempt the following questions: (14)

- a) Mesh analysis is applicable for
(a) Planar network (b) Non-Planar network (c) Both planar and non planar network (d) None of the above
- b) Kirchhoff second law is based on law of conservation of
(a) energy (b) charge (c) flux (d) Momentums
- c) To apply reciprocity theorem response to excitation ratio is
(a) ohms or mho (b) mho (c) ohm (d) None of the above
- d) Super position theorem is not applicable for
(a) current calculations (b) voltage calculations (c) power calculations (d) None of the above
- e) In an electric circuit, the dual of resistance is
(a) conductance (b) inductance (c) open circuit (d) short circuit
- f) Maximum power transfer theorem finds application in
(a) power circuits (b) distribution circuits (c) communications circuits (d) both power and communication
- g) What is an impulse Function?
- h) Thevenins resistance R_{th} is found
(a) By removing voltage source (b) Between some open terminals (c) between any two terminal (d) All of the above
- i) Steady state response is obtained from the transient response by substituting
(a) $t=0$ (b) $t = -\infty$ (c) $t = 1$ (d) $t = \infty$
- j) A dependent source
(a) may be a current source or a voltage source (b) is always a voltage source (c) is always a current source (d) is neither a current source nor a voltage source.
- k) Millman's theorem yield
(a) equivalent voltage & current source (b) equivalent impedance (c) equivalent resistance (d) All of the above
- l) In a Series R-L circuit voltage across resistor and inductor are 3 V & 4 V respectively then what is applied voltage?
(a) 7 V (b) 5 V (c) 4V (d) 12 V
- m) For a steady current inductor acts as



- (a) short circuit (b) open circuit (c) voltage circuit (d) current circuit
- n) If two resistors have same voltage drop in a series circuit it means
 (a) they are equal value (b) they are connected in parallel (c) they are equal (d) They are unequal

Attempt any four questions from Q-2 to Q-8

Q-2 Attempt all questions (14)

- (a) Explain the poles and zeros of the network function. State its important features. (07)
 (b) Explain the terms (i) Non-Linear (ii) Uni-lateral (iii) Passive (iv) Reciprocal (07)
 (v) Time variant (vi) Lumped parameter and (vii) Dual with reference to Network.

Q-3 Attempt all questions (14)

- (a) Find the Power delivered by the voltage source and the current in the 10Ω resistor for the circuit of Fig.1 (07)

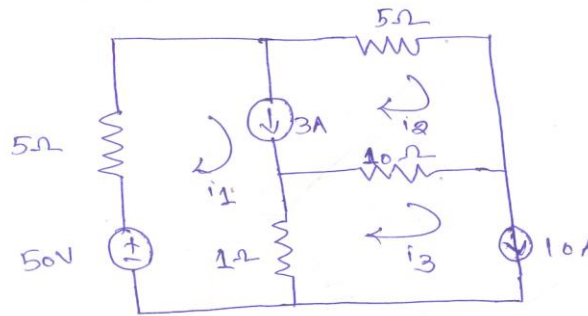


Fig - 1

- (b) Using nodal analysis to find the voltage across 5Ω resistor in the network shown in fig.2 (07)

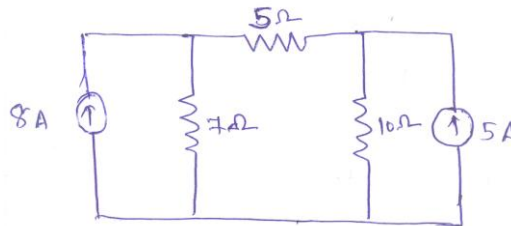


Fig. 2

Q-4 Attempt all questions (14)

- (a) Explain following terms of graph in network terminology with suitable example. (05)
 (i) Tree (ii) Twing (iii) Link (iv) Co-tree (v) Incidence Matrix
 (b) For the graph shown in fig.3 write the incidence matrix, tie set matrix and f-cut set matrix. (05)



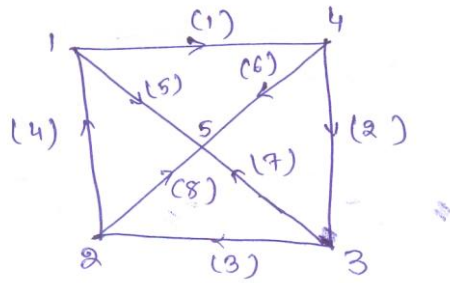


Fig - 3

(c) Write a short note on coefficient of coupling. (04)

Q-5 **Attempt all questions** (14)

(a) Find the step response for RLC series circuit (05)

(b) State maximum power transfer theorem and obtain proof of maximum power transfer theorem. (05)

(c) Explain source transformation. (04)

Q-6 **Attempt all questions** (14)

(a) Explain following in Brief: Ideal and Practical Energy source. (05)

(b) Find the Norton's equivalent circuit across a-b for the network shown in Fig 4. (05)

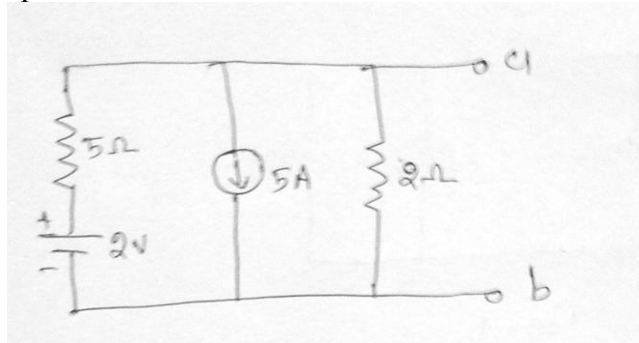


Fig.4

(c) Find the pole-zero plot of transform impedance of the network as shown in Fig.5 (04)

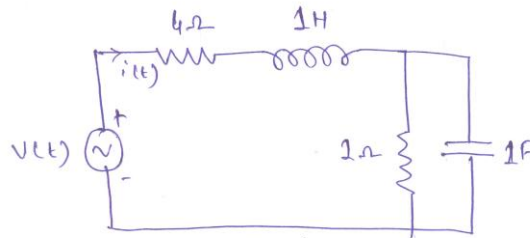


Fig-5

Q-7 **Attempt all questions** (14)

(a) For the network of Fig.6 find Z-parameter. (07)



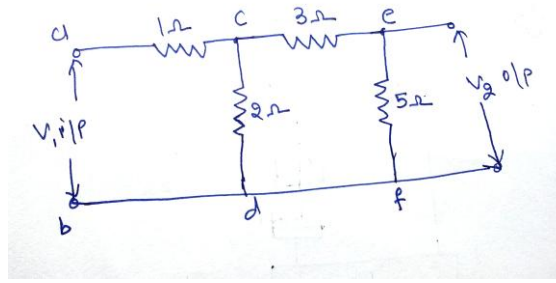


Fig.6

Q-8

- (b) Find the relation between Y parameter and Z- parameter & also find Vice-Versa. (07)
Attempt all questions (14)
 (a) In the given network of Fig.7 the switch k is opened at $t=0$. Solve for v , $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$ at $t=0^+$ if $I=10$ A, $R=10\Omega$ and $L=1$ H. (07)

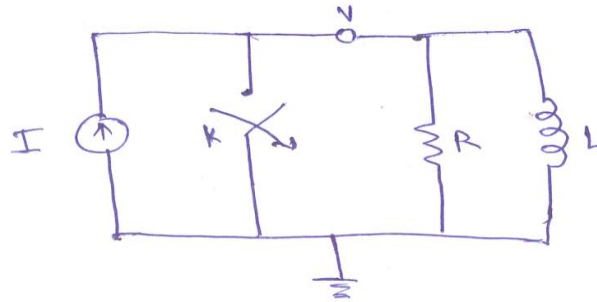


Fig - 7

- (b) For the network shown in Fig.8 the switch k is open for a long time and is closed at $t = 0$. Find $v_c(t)$. (07)

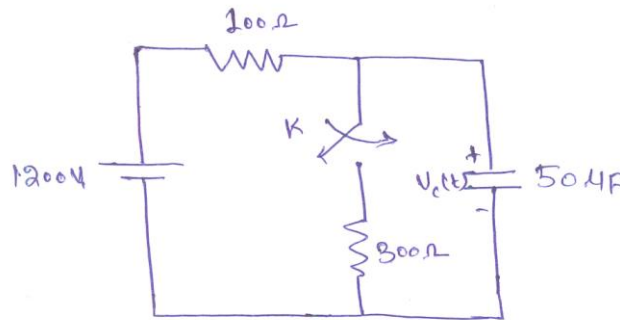


Fig - 8

