

C.U.SHAH UNIVERSITY**Summer Examination-2019****Subject Name: Power Electronics-I****Subject Code: 4TE05PEL1****Branch: B.Tech (Electrical)****Semester: 5****Date: 14/03/2019****Time: 10:30 To 01:30****Marks: 70**

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1**Attempt the following questions:****(14)**

- 1) Give any two characteristics of an ideal switch.
- 2) Draw the symbol of TRIAC and its V-I characteristics.
- 3) MOSFET is a _____ controlled device
- 4) Which power electronic converter is also known as frequency changer?
- 5) Draw the symbol of DIAC and its V-I characteristics.
- 6) How many junctions exist in an SCR?
- 7) What is the function of free wheeling diode in a phase controlled rectifier circuit?
- 8) Define: Latching current
- 9) An AC voltage controller converts fixed ac frequency into variable frequency. Determine whether the given statement is true or false.
- 10) Which power electronics device has lowest turn on and turn off time?
- 11) Ripple component in a six pulse converter is less compare to three pulse converter. Determine whether the given statement is true or false.
- 12) Give any two difference between 180° conduction mode and 120° conduction mode for 3-phase inverter.
- 13) Which power electronics converter converts a fixed DC voltage into a variable DC voltage?
- 14) Which device in the thyristor family turns off by applying a negative gate pulse?

Attempt any four questions from Q-2 to Q-8**Q-2****Attempt all questions****(14)**

- (a) Draw the V-I Characteristics of SCR. Explain the forward blocking and forward conduction operation of SCR **07**
- (b) Draw the structure of power diode, compare its structure and static V-I characteristics with signal diode. What are the advantages of power diode over signal diode? **07**
- Q-3 Attempt all questions (14)**
- (a) Draw the circuit diagram and explain the operation of single phase half wave controlled rectifier with resistive load. Draw the waveforms of supply voltage, load voltage and load current **07**
- (b) Draw the circuit diagram of single phase full wave bridge controlled rectifier with resistive load and explain its operation. Draw the waveforms of supply voltage, load current and load voltage **07**
- Q-4 Attempt all questions (14)**
- (a) Draw the circuit diagram of a step down chopper and explain its operation. Derive the equation of output voltage for a step down chopper. **07**
- (b) A 230 V (rms), 50 Hz single phase full wave bridge controlled rectifier is feeding a resistive load of 470 Ω . If the firing angle of SCR is $\alpha = 30^\circ$, Determine **07**
- i) Average load voltage ii) RMS load voltage
- Q-5 Attempt all questions (14)**
- (a) Draw the circuit diagram of single phase AC voltage controller with resistive load and explain its operation. Draw the waveforms of supply voltage, load voltage and load current. **07**
- (b) Draw the circuit diagram of UJT firing circuit and explain its operation with necessary waveforms. **07**
- Q-6 Attempt all questions (14)**
- (a) A single phase voltage controller has input voltage of 230 V, 50 Hz and a load of $R = 15 \Omega$. If the firing angle of SCR $\alpha = 45^\circ$, Determine **07**



i) RMS output voltage ii) Input power factor

- (b) Explain how does a freewheeling diode improves the input power factor in a controlled rectifier circuit with inductive load. **07**

Q-7 **Attempt all questions** **(14)**

- (a) Draw the circuit diagram and waveforms of single half bridge inverter with R-L load and explain its operation. **07**

- (b) Draw the circuit diagram and waveforms of single fullbridge inverter with resistive load and explain its operation. **07**

Q-8 **Attempt all questions** **(14)**

- (a) Draw only the circuit diagram, waveforms of gate pulse, phase voltage for three phase inverter with 180° conduction mode for resistive load. **07**

- (b) Draw the circuit diagram of single phase to single phase cyclo-converter with resistive load and explain its operation with necessary waveforms. **07**

