

C.U.SHAH UNIVERSITY

Summer Examination-2019

Subject Name: Power Electronics II**Subject Code: 4TE07PEL1****Branch: B.Tech (Electrical)****Semester: 7****Date: 11/03/2019****Time: 10:30 To 01:30****Marks: 70**

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1 Attempt the following questions: (14)

- 1) For a buck converter to reduce the conduction losses in diode.....
 - A) high on - resistance switch can be added in parallel
 - B) low on - resistance switch can be added in parallel
 - C) A high on - resistance switch can be added in series
- 2) The magnitude of output voltage at duty cycle $D=1$ for a practical BOOST converter is infinite.
 - A) True B) False
- 3) For a BOOST converter, input voltage = 25 V, duty cycle $D=0.5$, then output voltage is _____
 - A) 50 V B) 12.5 V C) 25 V D) 75 V
- 4) A forward converter is also known by an isolated _____ converter.
 - A) Boost B) Buck C) Buck-Boost D) None of the above
- 5) The output voltage equation for a flyback converter is $V_o =$ _____
 - A) $\frac{N_2}{N_1} DV_{in}$ B) $\frac{N_2}{N_1} \frac{1}{1-D} V_{in}$ C) $\frac{N_2}{N_1} \frac{1}{D} V_{in}$ D) $\frac{N_2}{N_1} \frac{D}{1-D} V_{in}$
- 6) The number of DC sources required for a Five level cascaded H Bridge inverter is _____
 - A) One B) Five C) Two D) Three
- 7) The number of clamping diodes required in a three level diode clamped inverter with one leg is _____
 - A) Three B) Five C) Four D) Two



- 8) Which one of the below given harmonic order gets eliminated in a six pulse diode rectifier?
 A) Third B) Fifth C) Seventh D) Eleventh
- 9) In a Delta/Z-1(Zigzag) transformer the secondary line voltage lags the primary line voltage.
 A) True B) False
- 10) If a hybrid stepper motor has a rotor pitch of 36° and a step angle of 9° , the number of its phases must be.....
 A) 4 B) 2 C) 3
- 11) Give any two advantages of multilevel inverter over two level inverter.
- 12) Define resonant converter?
- 13) Which of the following phase switching sequence represents half-step operation of a VR stepper motor.....
 A) A, B, C, A.... B)AB, BC, CA, AB.... C) A, AB, B, BC...
- 14) Percentage THD for cascaded H-bridge inverter is.....
 24.4% B) 60% C) 3% .

Attempt any four questions from Q-2 to Q-8

- Q-2 Attempt all questions (14)**
- (a) Explain overlapping and non-overlapping mode of operation in the case of full bridge series resonant inverter with bidirectional switches. **07**
- (b) Explain two Quadrant ZVS resonant converter. Support the answer with necessary circuit and waveforms. **07**
- Q-3 Attempt all questions (14)**
- (a) Draw the circuit diagram of buck converter and explain its operation with necessary waveforms
- (b) Draw the block diagram of ON LINE UPS and explain the function of each block. **07**
- Q-4 Attempt all questions (14)**
- (a) Explain 3-level diode clamped capacitor and advantage and disadvantage. **07**
- (b) Explain operation of push-pull converter with waveform. **07**
- Q-5 Attempt all questions (14)**
- (a) Draw the circuit diagram of five level flying capacitor inverter with one leg and explain its operation. Draw the output voltage waveform of five level inverter **07**
- (b) Explain Bidirectional AC power supplies with diagram **07**
- Q-6 Attempt all questions (14)**
- (a) Explain construction and working of stepper motor drive. **07**
- (b) Drive the equation for DC-link capacitor voltage balancing. **07**
- Q-7 Attempt all questions (14)**
- (a) Draw the circuit diagram 12-pulse series type diode rectifier. With the help of Fourier series equation and harmonic spectrum explain which individual harmonics **07**



gets eliminated in this rectifier.

- (b) Draw and explain the structure of Switched Reluctance Motor (SRM). **07**
- Q-8** **Attempt all questions** **(14)**
- (a) Draw the circuit diagram and waveforms of three phase half wave Brushless DC motor drive and explain its operation. **07**
- (b) Draw the circuit diagram and waveforms of CLASS E resonant inverter and explain its operation. **07**

