



- A)  $e_1$  leads  $e_2$  by  $\phi$  B)  $e_2$  lags  $e_1$  by  $\phi$  C)  $e_2$  leads  $e_1$  by  $\phi$  D)  $e_1$  is in phase with  $e_2$
- 10) At higher frequencies, the value of capacitive reactance\_\_\_\_\_
- A) Decreases B) Remains same C) Increases D) Depends on applied voltage
- 11) In series RLC circuit what is the power factor just below the resonance frequency?
- A) Lagging B) Leading C) Unity D) Zero
- 12) In a balanced 3-phase delta connected system, Line voltage is equal to Phase Voltage.
- A) True B) False
- 13) A transformer transforms\_\_\_\_\_.
- A) Voltage B) Current C) Frequency D) Voltage and Current
- 14) For a step up transformer, transformation ratio K is \_\_\_\_\_
- A) =0 B) >1 C) =1 D) < 1

**Attempt any four questions from Q-2 to Q-8**

- Q-2 Attempt all questions (14)**
- (a) Define temperature co-efficient of resistance. Prove that  $\alpha_t = \frac{\alpha_0}{1 + \alpha_0 t}$ , where  $\alpha_0 =$  (07)  
temperature co-efficient of resistance at 0° C.
- (b) Explain the effect of temperature on the resistance of the following. (07)
- i) Pure metals ii) Semiconductors  
iii) Electrolytes iv) Insulators
- Q-3 Attempt all questions (14)**
- (a) State Faraday's first law and second law electromagnetic induction. Derive the (07)  
equation of induced emf  $e = N \frac{d\phi}{dt}$ . Where N= Number of turns in a coil,  $\phi$  = flux in  
the coil.
- (b) Derive the expression of inductance for the coupled coil connected in series (07)
- Q-4 Attempt all questions (14)**
- (a) Define capacitance. Derive an expression of total capacitance for  $n$  number of (07)  
capacitors when connected in series.
- (b) Derive the expression of energy  $E = \frac{1}{2} CV^2$  stored in a electric field of the (07)  
capacitor. Where, C=capacitance of capacitor, V= Voltage across the capacitor.



