



Q-7 Attempt all questions (14)

(a) The 741 IC op-amp having the following parameter is connected as a non-inverting amplifier with $R_1 = 470\Omega$ and $R_F = 4.7K\Omega$: **07**

Open Loop Gain $A = 400,000$ Input Impedance $= 33M\Omega$

Output Impedance $R_o = 60\Omega$ Unity Gain Bandwidth $f_o = 0.6MHz$

Compute: i) Gain with Feedback A_F

ii) Input Impedance with Feedback R_{iF}

iii) Output Impedance with Feedback R_{oF}

iv) Bandwidth with Feedback f_F

(b) Draw the circuit diagram and waveforms of schmitt trigger circuit and explain its operation. Give the equations for upper threshold voltage and lower threshold voltages. **07**

Q-8 Attempt all questions (14)

(a) Draw the circuit diagram of first order low pass filter circuit and explain its operation. Draw the response gain versus frequency. **07**

(b) Draw the circuit diagram of wide band pass filter circuit and explain its operation. Draw the response gain versus frequency. **07**

