

Enrollment No: _____

Exam Seat No: _____

C.U.SHAH UNIVERSITY

Summer Examination-2019

Subject Name: Power Electronics

Subject Code: 4TE06PEL1

Branch: B.Tech (IC)

Semester: 6

Date: 29/04/2019

Time: 10:30 To 01:30

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1

Attempt the following questions:

(14)

- 1) Draw the symbol of MOSFET and GTO.
- 2) How many junction exists in an SCR?
- 3) Define: Latching Current.
- 4) Reverse voltage blocking capability of power diode is more compare to the signal diode. Determine whether the given statement is True or False.
- 5) Which one of the power electronics converter is used to convert fixed frequency into variable frequency?
- 6) How many power switches are used in single phase half bridge inverter?
- 7) In a full wave bridge rectifier with inductive load, if a freewheeling diode is connected across the load, the power factor gets improved. Determine whether the given statement is True or False.
- 8) Which one of the power electronics converter is used to convert fixed DC voltage into variable DC voltage?
- 9) If the firing angle of the SCR increases, the output voltage of the rectifier decreases. Determine whether the given statement is true or false.
- 10) Which one of the power semiconductor switch from a thyristor family is a bidirectional switch?
- 11) Give the types of thyristor commutation techniques.
- 12) If the gate current through the gate terminal of SCR increases, forward break voltage of SCR decreases. Determine whether the given statement is True or False.



- 13) List the turn on methods of SCR.
- 14) Give any four industrial applications of power electronics.

Attempt any four questions from Q-2 to Q-8

- Q-2** **Attempt all questions** **(14)**
- a) Draw the basic structure of power diode and explain its operation with the help of its V-I characteristics. **07**
- b) Draw the structure and V-I characteristics of IGBT and explain its operation. **07**
- Q-3** **Attempt all questions** **(14)**
- a) Explain the following modes of operation for SCR with help of its V-I characteristics. **07**
- i) Forward blocking mode
- ii) Forward conduction mode
- b) Draw the circuit diagram and waveforms of single phase half wave controlled rectifier with resistive load and explain its operation. **07**
- Q-4** **Attempt all questions** **(14)**
- a) Draw the circuit diagram and waveforms of single phase full wave diode rectifier with resistive load and explain its operation. **07**
- b) A step down dc chopper has a resistive load of $R = 15 \Omega$ and input voltage $E_{dc} = 200 V$. When the chopper switch remains ON its voltage drop is $0 V$. The chopper frequency is $1 kHz$. If the duty cycle is 50% , Determine, **07**
- i) Average output voltage
- ii) RMS output voltage
- iii) DC output power
- Q-5** **Attempt all questions** **(14)**
- a) Draw the circuit diagram and waveforms of single phase to single phase cyclo-converter for resistive load and explain its operation. **07**
- b) Draw the block diagram of off-line UPS and explain its operation. **07**
- Q-6** **Attempt all questions** **(14)**
- a) Draw the circuit diagram of a step down chopper and explain its operation. **07**
- b) Draw the circuit diagram and waveforms of single phase half bridge inverter with resistive load and explain its operation. **07**
- Q-7** **Attempt all questions** **(14)**
- a) Draw the circuit diagram of class B chopper and explain its operation. **07**



b) Explain how snubber circuit is useful in over voltage protection for thyristor. **07**

Q-8 **Attempt all questions** **(14)**

a) Draw the circuit diagram and waveforms of three phase to single phase cyclo-converter for resistive load and explain its operation. **07**

b) Draw the circuit diagram and waveforms of single phase full bridge inverter with *R-L* load and explain its operation. **07**

