

- A) e_1 leads e_2 by ϕ B) e_2 lags e_1 by ϕ C) e_2 leads e_1 by ϕ D) e_1 is in phase with e_2
- 10) At higher frequencies, the value of capacitive reactance_____
- A) Decreases B) Remains same C) Increases D) Depends on applied voltage
- 11) In series RLC circuit what is the power factor just below the resonance frequency?
- A) Lagging B) Leading C) Unity D) Zero
- 12) In a balanced 3-phase delta connected system, Line voltage is equal to Phase Voltage.
- A) True B) False
- 13) A transformer transforms_____.
- A) Voltage B) Current C) Frequency D) Voltage and Current
- 14) For a step up transformer, transformation ratio K is _____
- A) =0 B) >1 C) =1 D) < 1

Attempt any four questions from Q-2 to Q-8

- Q-2 Attempt all questions (14)**
- (a) Define temperature co-efficient of resistance. Prove that $\alpha_t = \frac{\alpha_0}{1 + \alpha_0 t}$, where $\alpha_0 =$ (14)
temperature co-efficient of resistance at 0°C . (07)
- (b) Explain the effect of temperature on the resistance of the following. (07)
- i) Pure metals ii) Semiconductors
iii) Electrolytes iv) Insulators
- Q-3 Attempt all questions (14)**
- (a) State Faraday's first law and second law electromagnetic induction. Derive the (07)
equation of induced emf $e = N \frac{d\phi}{dt}$. Where N= Number of turns in a coil, ϕ = flux in
the coil.
- (b) Derive the expression of inductance for the coupled coil connected in series (07)
- Q-4 Attempt all questions (14)**
- (a) Define capacitance. Derive an expression of total capacitance for n number of (07)
capacitors when connected in series.
- (b) Derive the expression of energy $E = \frac{1}{2} CV^2$ stored in a electric field of the (07)
capacitor. Where, C=capacitance of capacitor, V= Voltage across the capacitor.



