

C.U.SHAH UNIVERSITY

Summer Examination-2019

Subject Name :Analog and Digital Electronics

Subject Code :5SC01ADE1

Branch: M.Sc. (Physics)

Semester : 1

Date :19/03/2019

Time : 02:30 To 05:30

Marks : 70

Instructions:

- (1) Use of Programmable calculator and any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

SECTION – I

- Q-1 Attempt the Following questions (07)**
- a. What is a reverse recovery time of diode?
 - b. Differentiate between UTP and LTP.
 - c. What is meant by precision rectifier?
 - d. Define photo-detectors.
 - e. Write applications of photodiode.
 - f. What is a comparator?
 - g. What is an optocoupler? Write its applications.
- Q-2 Attempt all questions (14)**
- a. What do you mean by clipper? Explain briefly positive and negative peak clipper circuits using diode with suitable diagrams. (07)
 - b. What is LDR? Give its construction and characteristics. How an LDR can be used as an overlight detector? (07)
- OR**
- Q-2 Attempt all questions (14)**
- a. What is clamper? Explain briefly positive and negative peak clamping circuits using diode with neat and clean diagrams. (07)
 - b. What is LED? Give its principle of working, construction and write its applications. (07)
- Q-3 Attempt all questions (14)**
- a. Discuss how an OPAMP can be made to act as an astable multivibrator? Obtain an expression for frequency of oscillations. (07)
 - b. What is the difference between a basic comparator and the Schmitt trigger? Explain briefly. (07)
- OR**
- Q-3 a. Describe OPAMP circuit for bistable multivibrator. Explain their operations. (07)**
- b. Write short notes on switching applications of OPAMP and OPAMP inverter. (07)**



SECTION – II

- Q-4** **Attempt the Following questions** **(07)**
- a. Which type of amplifiers operate with least distortion?
 - b. What type of bias is used in a true class B push-pull amplifier?
 - c. State common difference between voltage and power amplifiers.
 - d. What is a tuned amplifier?
 - e. Write full name of DAC and ADC.
 - f. What do you mean by binary ladder?
 - g. How counters can be used for the measurement of frequency?
- Q-5** **Attempt all questions** **(14)**
- a. State clearly the meaning of class A, B and C as applied to power amplifiers. **(07)**
What is meant by ‘angle of flow’?
 - b. Draw the circuit of a class B push-pull amplifier and explain its operation. Derive an expression for its maximum conversion efficiency. **(07)**
- OR**
- Q-5** a. Explain briefly class A power amplifier. How power is distributed in it? **(07)**
- b. What do you mean by double tuned amplifier? Show that in case of double tuned amplifier the 3dB bandwidth exceeds that a single tuned amplifier. **(07)**
- Q-6** **Attempt all questions** **(14)**
- a. Describe the operation of half and full adder with suitable diagram. What is parallel adder? **(07)**
 - b. Write notes on multiplexers and de-multiplexers. **(07)**
- OR**
- Q-6** **Attempt all Questions** **(14)**
- a. Explain the various types of memory and their merits and demerits. **(07)**
 - b. What do you understand by sequential and combinational logic circuits? Describe the operation of S-R latch. **(07)**

