

Enrollment No: \_\_\_\_\_

Exam Seat No: \_\_\_\_\_

# C.U.SHAH UNIVERSITY

## Summer Examination-2019

**Subject Name: Analog and Digital Electronics**

**Subject Code: 4SC04ADE1**

**Branch: B.Sc. (All)**

**Semester: 4**

**Date: 03/05/2019**

**Time: 02:30 To 05:30**

**Marks: 70**

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
  - (2) Instructions written on main answer book are strictly to be obeyed.
  - (3) Draw neat diagrams and figures (if necessary) at right places.
  - (4) Assume suitable data if needed.
- 

<b>Q-1</b>	<b>Attempt the following questions:</b>	<b>(14)</b>
	a) Differentiate: Analog and Digital Signal	1
	b) What do you mean by stabilization in a transistor?	1
	c) Define the term Virtual Ground in Op Amp.	1
	d) List two advantages of JFET.	1
	e) Define Thermistor.	1
	f) What is an Op-Amp?	1
	g) Write the Commutative laws used in logic gates.	1
	h) What is CMRR in Op-AMP operation?	1
	i) List the names of the basic logic gates.	1
	j) Give full form of MOSFET and draw its symbol.	1
	k) Draw the diagram for Op Amp when it is used as an Integrator.	1
	l) Define pinch-off voltage.	1
	m) Give the truth table for NOR gate.	1
	n) Give two applications of Op-Amp	1

**Attempt any four questions from Q-2 to Q-8**

<b>Q-2</b>	<b>Attempt all questions</b>	<b>(14)</b>
	a) Discuss in detail transistor as an amplifier in CE configuration.	6
	b) Enumerate on the working and construction of MOSFET.	8
<b>Q-3</b>	<b>Attempt all questions</b>	<b>(14)</b>
	a) Explain in detail the terms Load Line and Operating Point in Transistor working.	8
	b) Write a note on construction and working of a JFET.	6
<b>Q-4</b>	<b>Attempt all questions</b>	<b>(14)</b>
	a) Describe the input and output characteristics of Common Base Transistor connection.	7
	b) Define Stability factor of a transistor, also derive the formula for the same.	7
<b>Q-5</b>	<b>Attempt all questions</b>	<b>(14)</b>
	a) Explain AND gate in detail	6



- Q-6**
- b) Discuss the characteristics of an Ideal Operational Amp **8**
- Attempt all questions** **(14)**
- a) Write a note on NAND as a Universal Gate. **6**
- b) Convert the following decimals to binary **8**
- (i)  $15_{10}$
- (ii)  $0.3125_{10}$
- Q-7** **Attempt all questions** **(14)**
- a) State and Prove De Morgan's Theorem used in Logic Gates. **7**
- b) Discuss in detail on Op Amp used as an Adder. **7**
- Q-8** **Attempt all questions** **(14)**
- a) Simplify the Boolean Expressions: **8**
- $Y = (A + B + C).(A + B)$
- $Y = AB + \overline{AC} + A\overline{B}C(AB + C)$
- b) Explain in detail Op Amp as an Inverting Amplifier. **6**

