



- Q-4**      **Attempt all questions**      **(14)**
- a) Explain in detail voltage divider biasing technique with circuit diagram.      **07**
  - b) Draw the h-parameter equivalent circuit of Common Emitter Amplifier circuit and derive the expression for input impedance, output impedance, voltage gain and current gain.      **07**
- Q-5**      **Attempt all questions**      **(14)**
- a) Explain with a diagram, the working of a transformer coupled class AB power amplifier.      **07**
  - b) Explain with a diagram, the working of a class C power amplifier.      **07**
- Q-6**      **Attempt all questions**      **(14)**
- a) Derive the formula of voltage gain for op-amp inverting and non-inverting amplifier.      **07**
  - b) Explain in detail integrator using Op-Amp with neat circuit diagram.      **07**
- Q-7**      **Attempt all questions**      **(14)**
- a) Explain in detail voltage shunt feedback amplifier with circuit diagram.      **07**
  - b) Explain with the help of circuit diagram working of RC phase shift oscillator.      **07**
- Q-8**      **Attempt all questions**      **(14)**
- a) Explain in detail current shunt feedback amplifier with circuit diagram.      **07**
  - b) Explain with the help of circuit diagram working of crystal oscillator.      **07**

