

C.U. SHAH UNIVERSITY

Winter Examination-2019

Subject Name: Power Electronics-I

Subject Code: 4TE05PEL1

Branch: B.Tech (Electrical)

Semester: 5

Date: 16/11/2019

Time: 10:30 To 01:30

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1

Attempt the following questions:

(14)

- 1) Give any two differences between signal diode and power diode.
- 2) Draw the symbol of IGBT and DIAC.
- 3) Define: Latching Current.
- 4) For an SCR Holding current (I_H) < Latching Current (I_L) Determine whether the given statement is TRUE or FALSE.
- 5) Which power electronic switch is used in high frequency applications?
- 6) Give any two turn on methods of SCR.
- 7) What is the purpose of using freewheeling diode at the output side of the rectifier?
- 8) Ripple factor in a three phase full bridge rectifier is smaller than single phase full wave bridge rectifier. Determine whether the given statement is TRUE or FALSE.
- 9) How many SCR are required in a three phase half bridge controlled rectifier?
- 10) Give the principle of an inverter.
- 11) What is the difference between single phase half bridge inverter and single phase full bridge inverter from construction point of view?
- 12) Give any two difference between 3 phase inverter with 180° and 120° conduction mode.
- 13) Which power electronic converter converts fixed AC voltage into variable AC voltage?
- 14) In a step down DC to DC converter, output voltage is greater than input voltage.



controller with resistive load and explain its operation.

- (b) Draw the circuit diagram and waveforms of two stage sequence control AC voltage controller with resistive load and explain its operation. **07**

Q-8

Attempt all questions (14)

- (a) Draw the circuit diagram and waveforms of single phase to single phase cyclo-converter for resistive load and explain its operation. **07**

- (b) A single phase half wave controlled rectifier feeds a load of $R = 75 \Omega$ with an input voltage of $230 V, 50 Hz$ supply. Firing angle for thyristor is 45° . Calculate **07**

- i) RMS value of output voltage
- ii) Average value of output voltage

