

# C.U.SHAH UNIVERSITY

## Winter Examination-2019

**Subject Name: Power Electronics II****Subject Code: 4TE07PEL1****Branch: B.Tech (Electrical)****Semester : 7****Date : 13/11/2019****Time : 10:30 To 01:30****Marks : 70****Instructions:**

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
  - (2) Instructions written on main answer book are strictly to be obeyed.
  - (3) Draw neat diagrams and figures (if necessary) at right places.
  - (4) Assume suitable data if needed.
- 

**Q-1****Attempt the following questions:****(14)**

- 1) The DC-DC converter should be operated at a very low switching frequency.  
A) True B) False
- 2) In a Buck converter if,  $T_{on} = 1\mu s$ ,  $T_{off} = 2\mu s$ , then duty cycle  $D =$  \_\_\_\_\_.  
A)  $0.5 \mu s$  B)  $2 \mu s$  C)  $0.33 \mu s$  D)  $3 \mu s$
- 3) In a steady state operation of DC-DC converter average voltage across the inductor is \_\_\_\_\_.  
A) Finite B) Zero
- 4) A flyback converter is also known by an isolated \_\_\_\_\_ converter.  
A) Boost                      B) Buck                      C) Buck-Boost                      D) None of the above
- 5) The output voltage equation for a flyback converter is  $V_o =$  \_\_\_\_\_.  
A)  $\frac{N_2}{N_1} D V_{in}$                       B)  $\frac{N_2}{N_1} \frac{1}{1-D} V_{in}$                       C)  $\frac{N_2}{N_1} \frac{1}{D} V_{in}$                       D)  $\frac{N_2}{N_1} \frac{D}{1-D} V_{in}$
- 6) The number of DC sources required for a Five level cascaded H Bridge inverter is \_\_\_\_\_.  
A) One                      B) Five                      C) Two                      D) Three
- 7) The number of clamping diodes required in a three level diode clamped inverter with one leg is \_\_\_\_\_.  
A) Three                      B) Five                      C) Four                      D) Two
- 8) Which one of the below given harmonic order gets eliminated in a six pulse diode rectifier?  
A) Third                      B) Fifth                      C) Seventh                      D) Eleventh
- 9) The number of switches used in a half bridge push pull converter is \_\_\_\_\_.  
A) 4 B) 1 C) 2 D) 6
- 10) If a hybrid stepper motor has a rotor pitch of  $36^\circ$  and a step angle of  $9^\circ$ , the number of its phases must be.....  
A) 4                      B) 2                      C) 3



- 11) Give any two advantages of multilevel inverter.
- 12) Define resonant converter?
- 13) Which of the following phase switching sequence represents half-step operation of a VR stepper motor.....  
A) A, B, C, A.... B) AB, BC, CA, AB.... C) A, AB, B, BC...
- 14) Percentage THD for cascaded H-bridge inverter is.....  
24.4% B) 60% C) 3% .

**Attempt any four questions from Q-2 to Q-8**

- |            |   |             |
|------------|---|-------------|
| <b>Q-2</b> | <b>Attempt all questions</b>  | <b>(14)</b> |
|            | (a) Draw the circuit diagram of buck converter and explain its operation with necessary waveforms.  | <b>07</b>   |
|            | (b) Draw the block diagram of ON LINE UPS and explain the function of each block.   | <b>07</b>   |
| <b>Q-3</b> | <b>Attempt all questions</b>  | <b>(14)</b> |
|            | (a) Draw the circuit diagram and waveforms of CLASS E resonant inverter and explain its operation.  |             |
|            | (b) Explain operation of push-pull converter with waveform.   | <b>07</b>   |
| <b>Q-4</b> | <b>Attempt all questions</b>  | <b>(14)</b> |
|            | (a) Explain 3-level diode clamped capacitor and advantage and disadvantage.   | <b>07</b>   |
|            | (b) Draw the circuit diagram and waveforms of a FLYBACK converter and explain its operation.  | <b>07</b>   |
| <b>Q-5</b> | <b>Attempt all questions</b>  | <b>(14)</b> |
|            | (a) Explain ZVS resonant converter with Waveform.   | <b>07</b>   |
|            | (b) Explain Bidirectional AC power supplies with diagram  | <b>07</b>   |
| <b>Q-6</b> | <b>Attempt all questions</b>  | <b>(14)</b> |
|            | (a) Explain Single Phase Parallel resonant inverter circuit diagram with waveform.  | <b>07</b>   |
|            | (b) A series resonance inverter with series loaded delivers a load power of $P_L = 1 \text{ kW}$ at resonance. The load resistance is $R = 10\Omega$ . The resonant frequency is $f_o = 20 \text{ kHz}$ . Find (a) the d.c. input voltage $V_s$ (b) Quality factor $Q_s$ if it is required to reduce the load power to 250 W by frequency control so that $u = 0.8$ (c) inductor L and (d) capacitor C. | <b>07</b>   |
| <b>Q-7</b> | <b>Attempt all questions</b>  | <b>(14)</b> |
|            | (a) Explain construction and working of stepper motor drive.  | <b>07</b>   |
|            | (b) Drive the equation for DC-link capacitor voltage balancing.   | <b>07</b>   |
| <b>Q-8</b> | <b>Attempt all questions</b>  | <b>(14)</b> |
|            | (a) Draw the circuit diagram and waveforms of three phase half wave Brushless DC motor drive and explain its operation.   | <b>07</b>   |
|            | (b) Explain Design of apparent transformer power for half bridge circuit.   | <b>07</b>   |

