

# C.U.SHAH UNIVERSITY

## Winter Examination-2019

**Subject Name: Power Electronics**

**Subject Code: 4TE06PEL1**

**Branch: B.Tech (IC)**

**Semester: 6**

**Date: 09/09/2019**

**Time: 10:30 To 01:30**

**Marks: 70**

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
  - (2) Instructions written on main answer book are strictly to be obeyed.
  - (3) Draw neat diagrams and figures (if necessary) at right places.
  - (4) Assume suitable data if needed.
- 

**Q-1    Attempt the following questions:    (14)**

- 1) Draw the symbol of DIAC and its V-I characteristics.
- 2) What is the junction voltage for a practical diode?
- 3) A rectifier converts AC power into \_\_\_\_\_ power.
- 4) How many junctions exist in a SCR?
- 5) How many thyristors are required in a full wave bridge rectifier?
- 6) Define: Holding Current
- 7) Draw the symbol of MOSFET and IGBT.
- 8) Which power electronic converter converts fixed DC voltage into variable DC voltage?
- 9) \_\_\_\_\_ power electronic converter converts DC power into AC power.
- 10) An SCR is a bidirectional device. Determine whether the given statement is TRUE or FALSE.
- 11) Give any two applications of power electronics.
- 12) Reverse voltage blocking capability of power diode is more compared to the signal diode. Determine whether the given statement is TRUE or FALSE.
- 13) If the current through the gate terminal of SCR increases, forward break voltage of SCR \_\_\_\_\_ (Increases/Decreases).
- 14) What is the importance of snubber circuit in power electronics?

**Attempt any four questions from Q-2 to Q-8**

**Q-2    Attempt all questions    (14)**

- a) Explain any three turn-on methods of thyristor. **07**
- b) Explain the following modes of operation for SCR with help of its V-I **07**



characteristics.

- i) Reverse blocking mode
- ii) Forward conduction mode

- Q-3** **Attempt all questions** (14)
- a) A 110 V (rms), 50 Hz single phase half wave controlled rectifier is feeding a resistive load of 250  $\Omega$ . If the firing angle of SCR is  $\alpha = 45^\circ$ , Determine (14)
- i) Average load voltage                  ii) DC Output Power (07)
- b) Draw the circuit diagram and waveforms of single phase full wave center tap rectifier with resistive load and explain its operation. (07)
- 
- Q-4** **Attempt all questions** (14)
- a) Draw the circuit diagram and waveforms of single phase half wave controlled rectifier with resistive load and explain its operation. (07)
- b) Draw the basic structure of power diode and explain its operation with the help of its V-I characteristics. (07)
- 
- Q-5** **Attempt all questions** (14)
- a) Draw the circuit diagram of a step up chopper and explain its operation. Derive the equation of output voltage for a step up chopper. (07)
- b) Draw the circuit diagram and waveforms of single phase half bridge inverter with resistive load and explain its operation. (07)
- 
- Q-6** **Attempt all questions** (14)
- a) Draw the block diagram of on-line UPS and explain its operation. (07)
- b) Draw the circuit diagram of class A chopper and explain its operation. (07)
- 
- Q-7** **Attempt all questions** (14)
- a) Draw the circuit diagram and waveforms of single phase full bridge inverter with resistive load and explain its operation. (07)
- b) Explain temperature controller using power electronics. (07)
- 
- Q-8** **Attempt all questions** (14)
- a) Draw the circuit diagram and waveforms of single phase to single phase cyclo-converter for resistive load and explain its operation. (07)
- b) Draw the circuit and waveforms of basic series inverter and explain its operation. (07)

