

Enrollment No: _____

Exam Seat No: _____

C. U. SHAH UNIVERSITY

Winter Examination-2020

Subject Name: Digital Circuits

Subject Code: 4TE03DCI1

Branch: B.Tech (Electrical)

Semester: 3

Date: 10/03/2021

Time: 11:00 To 02:00

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1 Attempt the following questions: (14)

- a) Which of these sets of logic gates are designated as universal gates?
 - a) NOR, NAND.
 - b) XOR, NOR, NAND.
 - c) OR, NOT, AND.
 - d) NOR, NAND, XNOR.
- b) Which of the following is a digital device?
 - a) Regulator of a fan
 - b) Microphone
 - c) Resistance of a material
 - d) Light switch
- c) If a Hexadecimal number needs to convert to binary. For each hexadecimal digit, there will be how many bits
 - a) 1
 - b) 2
 - c) 4
 - d) 8
- d) Complement of NOR and OR gate is _____ and _____ respectively.
 - a) AND, NAND
 - b) NAND, AND
 - c) NOR, OR
 - d) None of above
- e) When will be the output of an AND gate is LOW?
 - a) When any input is LOW
 - b) When any input is HIGH
 - c) When all inputs are HIGH
 - d) When all input is LOW
- f) Total number of inputs in a half adder is _____
 - a) 2



- b) 3
- c) 4
- d) 1
- g) The difference between half adder and full adder is _____
 - a) Half adder has two inputs while full adder has four inputs
 - b) Half adder has one output while full adder has two outputs
 - c) Half adder has two inputs while full adder has three inputs
 - d) All of the Mentioned
- h) In a number system, each position of a digit represents a specific power of the base.
 - a) True
 - b) False
- i) What does the symbol D represent in a hexadecimal number system?
 - a) 8
 - b) 16
 - c) 13
 - d) 14
- j) A bit in a computer terminology means either 0 or 1.
 - a) True
 - b) False
- k) The binary equivalent of the octal number $(0010010100)_2$ is _____
- l) Most significant bit of arithmetic addition is called
 - (a) overflow (b) carry (c) output (d) zero bit
- m) Code conversion circuits mostly uses
 - (a)AND-OR gates (b)AND gates (c)OR gates (d)XOR gates
- n) Two-bit subtraction is done by
 - (a) demux (b) mux (c) full subtract (d) half subtract

Attempt any four questions from Q-2 to Q-8

- | | | |
|------------|--|-------------|
| Q-2 | Attempt all questions | (14) |
| | (a) Compare digital system with analog system. | (07) |
| | (b) Give statement and explain De' morgens Theorem. | (07) |
| Q-3 | Attempt all questions | (14) |
| | (a) Design and Implement a Half Adder. | (07) |
| | (b) Draw the logic symbol and construct the truth table for all logic gates. | (07) |
| Q-4 | Attempt all questions | (14) |
| | (a) Write definition of Flip-flop and explain J-K flip flop. | (07) |
| | (b) Design and Implement a 3-line to 8-line decoder. | (07) |
| Q-5 | Attempt all questions | (14) |
| | (a) Explain full adder circuit with truth table. | (07) |
| | (b) With neat sketch explain the operation of R-S flip flop. | (07) |
| Q-6 | Attempt all questions | (14) |
| | (a) Convert $(10101)_2$ to decimal. | (07) |
| | Convert $(1001011)_2$ to decimal. | |
| | Convert $(105.15)_{10}$ to binary. | |



- Write 1st Complement of 1000101.
- (b) Convert (4BAC)₁₆ to binary. (07)
Convert (2598.675)₁₀ to hex.
Add to Numbers: 11011+10001.
Multiply (1101)₂ to by (110)₂.

Q-7 Attempt all questions (14)

- (a) Design and Implement a 1-line to 8-line demultiplexer. (07)
(b) What are the applications of shift register? (07)

Q-8 Attempt all questions (14)

- (a) Comparison of Counters and Registers. (07)
(b) With neat diagram explain the operation of 4- bit parallel- in Serial-out Shift register. (07)

