

C. U. SHAH UNIVERSITY

Summer Examination-2020

Subject Name: Linear Electronics

Subject Code: 4TE03LNE1

Branch: B.Tech (CE)

Semester : 3

Date : 29/02/2020

Time : 02:30 To 05:30

Marks : 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
- (2) Instructions written on main answer book are strictly to be obeyed.
- (3) Draw neat diagrams and figures (if necessary) at right places.
- (4) Assume suitable data if needed.

Q-1

Attempt the following questions

(14)

- a) A transistor has..... pn junctions.
A) 1 B) 2 C) 3 D) 4
- b) The element that has the largest size in a transistor is.....
A) Collector B) Base C) Emitter D) None
- c) The emitter of a transistor is doped.
A) Moderately B) Lightly C) Heavily D) None
- d) In a transistor, $I_C = 100$ mA and $I_E = 100.5$ mA. The value of β is
A) 100 B) 50 C) 200 D) None
- e) If the value of collector current I_C increases, then value of V_{CE}
A) remains same B) decreases C) increases D) None
- f) The operating point is also called the.....
A) Cut-off point B) Saturation point C) Quiescent point D) None
- g) If operating point is shifted towards..... point thencycle will be clipped
A) saturation, upper B) cut off, lower C) mid-point D) both A and B
- h) Transistor biasing represents..... Condition.
A) ac B) dc C) Both ac and dc D) None
- i) The stabilization of operating point in potential divider method is provided by.....
A) R_E consideration B) R_C consideration C) V_{CC} consideration D) None
- j) In class A amplifier, the operating point on d. c. load line.
A) Cut-off B) Middle C) Saturation D) None of above
- k) Input resistance of an ideal op-amp.....
A) high B) infinite C) medium D) low
- l) An open loop gain of an ideal op-amp.....
A) high B) low C) infinite D) medium
- m) In negative feedback phase difference between input and output is
A) 0 B) 180 C) 360° D) Both A and C
- n) Which oscillator has highest stability?
A) Colpitts B) Hartley C) Crystal D) None




Attempt any four questions from Q-2 to Q-8

Q-2 Attempt all questions 14

- (a) State different transistor connection circuits. Draw the CB circuit and derive the equation of current amplification factor α and collector current I_C . In a CB connection, α is 0.9. If the I_E is 1mA, determine the value of I_B . **07**
- (b) Derive the relationship between leakage currents (I_{CBO} and I_{CEO}) in terms of α and β . If $I_{CBO} = 0.2 \mu A$, $I_{CEO} = 20 \mu A$ and $I_C = 1mA$, find the value of α , β , I_E and I_B . **07**

Q-3 Attempt all questions

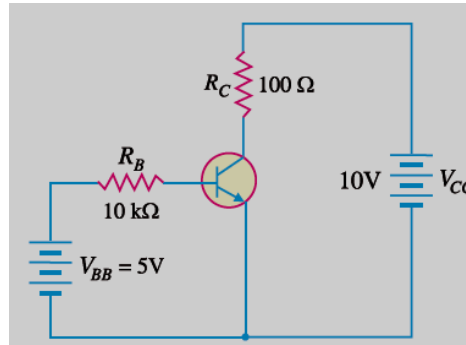- (a) Determine V_{CE} and V_{CB} in the transistor circuit shown in Figure below. The transistor is of silicon and has $\beta = 150$. **07**



- (b) Explain in detail dc load line and operating point with diagram for CE circuit. In CE circuit, if $V_{CC} = 12V$ and $R_C = 6 k\Omega$, draw the dc load line. What will be the Q point if zero signal base current is $20\mu A$ and $\beta = 50$? **07**

Q-4 Attempt all questions

- (a) What is faithful amplification? State and explain in detail with illustrations different conditions to be fulfilled to achieve faithful amplification in a transistor amplifier. **07**
- (b) Enlist different transistor biasing methods. Explain any one of them in detail with circuit diagram. **07**

Q-5 Attempt all questions

- (a) Explain with a diagram, the working of a class B push-pull power amplifier. **07**
- (b) Derive the equation for overall gain for positive and negative feedback. **07**

Q-6 Attempt all questions

- (a) Explain in detail inverting and non-inverting amplifier using Op-Amp with neat circuit diagrams. **07**
- (b) Explain in detail differentiator using Op-Amp with neat circuit diagram. **07**

Q-7 Attempt all questions

- (a) Draw and explain in detail voltage series feedback amplifier. **07**
- (b) Explain with the help of circuit diagram working of crystal oscillator. **07**

Q-8 Attempt all questions

- (a) Draw and explain in detail voltage shunt feedback amplifier. **07**
- (b) Explain with the help of circuit diagram working of Colpitts oscillator. **07**

