

Enrollment No: _____

Exam Seat No: _____

C.U.SHAH UNIVERSITY

Winter Examination-2021

Subject Name: Digital Electronics

Subject Code: 4TE03DEL1

Branch: B.Tech (CE)

Semester: 3

Date: 17/01/2022

Time : 11:00 To 02:00

Marks : 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
- (2) Instructions written on main answer book are strictly to be obeyed.
- (3) Draw neat diagrams and figures (if necessary) at right places.
- (4) Assume suitable data if needed.

- Q-1 Attempt the following questions: (14)**
- a) Define Quad word. 1
 - b) Find out binary Subtraction of $1010110 - 101010$ 1
 - c) 2nd complement of 0001 is 1
a) 1101 b) 0111 c) 1100 d) 1111
 - d) Solve $(1001)_2 = (?)_{10}$ 1
 - e) In Excess-3 code each coded number isthan in BCD code. 1
(a) Four larger (b) three smaller (c) three larger (d) much larger.
 - f) Find out 1st complement of 110011. 1
 - g) Find out 2nd complement of 1010. 1
 - h) What is Fan-out? 1
 - i) An AND gate has 4 inputs. The number of input words in its truth table are 1
(a) 4 (b) 16 (c) 64 (d) 128
 - j) 1st complement of 1101 1
a) 0010 b) 0101 c) 1100 d) 1111.
 - k) J-K Flip Flop derive from _____? 1
(a) T Flip Flop (b) R-S Flip Flop (c) D Flip Flop (d) None
 - l) Find out gray to binary number system of 1010. 1
 - m) How many Flip-Flops are required for mod-16 counter? 1
(a) 2 (b) 6 (c) 3 (d) 4
 - n) The number of control lines for a 16 – to – 1 multiplexer is 1
(a) 2 (b) 3 (c) 4 (d) 5

Attempt any four questions from Q-2 to Q-8

- Q-2 Attempt all questions (14)**
- (a) What is Logic Circuit? List out category of Logic gate. Explain Basic gate. 7
 - (b) Explain 2 to 4 line Decoder with proper circuit. 7
- Q-3 Attempt all questions (14)**
- (a) Prove associative law and distributive laws using truth table 7
 - (b) Explain clocked R-S flip flop. Explain disadvantage of R-S flip flop. 7



Q-4	Attempt all questions	(14)
(a)	Explain full adder with Truth table.	7
(b)	Draw circuit of Basic Gates using NAND & NOR Gates.	7
Q-5	Attempt all questions	(14)
(a)	What is Shift Register? Explain 8-bit Shift Register with proper circuit.	7
(b)	What is Karnaugh Map? Draw Structure of different types of k-map variable combination.	7
Q-6	Attempt all questions	(14)
(a)	Explain Master Slave Flip Flop with proper circuit.	7
(b)	What is Asynchronous Counter? Explain 4-bit Shift Counter.	7
Q-7	Attempt all questions	(14)
(a)	Write a note on Binary Ripple Counter.	7
(b)	What is Multiplexer? Explain 4 to 1 line Multiplexer.	7
Q-8	Attempt all questions	(14)
(a)	Explain SOP and Simplify $\sum(4,5,6,7,12,13,14,15)$.	7
(b)	Write notes on MOS and CMOS.	7

