

C. U. SHAH UNIVERSITY

Summer Examination-2022

Subject Name: Analog Electronics Circuits

Subject Code: 4TE03AEC1

Branch: B.Tech (Electrical)

Semester: 3

Date: 22/04/2022

Time: 02:30 To 05:30

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
- (2) Instructions written on main answer book are strictly to be obeyed.
- (3) Draw neat diagrams and figures (if necessary) at right places.
- (4) Assume suitable data if needed.

Q-1 Attempt the following questions: (14)

- a) Rectification Efficiency of Half Wave Diode Rectifier with R Load is _____%.
- b) Ripple Factor of Full Wave Diode Rectifier with R Load is _____.
- c) PIV for Diode Bridge Rectifier is _____ volts.
- d) CE Configuration of BJT is commonly used because -----.
- e) AC / DC Load lines decides _____ in amplifier.
- f) Voltage Regulated IC 7812 is used for _____ volts.
- g) Full Form of CMRR is _____ & PSRR is _____.
- h) Zero Crossing Detector circuit is one type of _____.
- i) Hartley oscillator is commonly used in _____.
- j) Oscillator Circuit needs _____ input(s).
- k) IC-555 is invariably used in applications such as -----.
- l) In phase shift oscillator, we use _____ RC sections.
- m) Slew Rate is the measurement of _____ in Op-amp.
- n) Filter Circuits block the ----- component & pass ----- component.

Attempt any four questions from Q-2 to Q-8

Q-2 Attempt all questions (14)

- a) Compare Diode with Bipolar Junction Transistor. (3)
- b) Give comparative statements in Tabular form for CE, CB, CC Configuration of BJT (4)
- c) Draw and explain Full Wave Rectifier circuit diagram and various waveforms having capacitor filter for R – Load. (7)

Q-3 Attempt all questions (14)

- a) Discuss Ideal Op-amp. (3)
- b) Discuss practical Op-amp Characteristics. (4)
- c) Draw the basic block diagram, symbol, characteristics and equivalent circuit of Operational Amplifier. List the type and important parameters of Op-amp. (7)



- Q-4 Attempt all questions (14)**
- a) Draw Class-C amplifier circuit and specify its applications. (3)
 - b) Draw Class – A amplifier circuit and specify its applications and limitations (4)
 - c) Explain 78xx and 79xx voltage regulators. Draw necessary circuit diagram to get 12-volt constant output using 7812 IC. (7)
- Q-5 Attempt all questions (14)**
- a) Discus fundamental of tuned amplifier. (3)
 - b) Discus the effect of bypass and coupling capacitors on frequency response of amplifier circuit. (4)
 - c) Explain basic inverting and non-inverting amplifier circuits using Op-amp (7)
- Q-6 Attempt all questions (14)**
- a) Discuss Phase Shift Oscillator. (3)
 - b) Discuss Wien Bridge Oscillator (4)
 - c) Draw and explain the circuit diagram and various waveforms for Triangular Wave Generator. (7)
- Q-7 Attempt all questions (14)**
- a) Discus general characteristics of negative feedback amplifier. (3)
 - b) Discus on Heat-sinks design. (4)
 - c) Draw and explain feedback amplifier. Deduce the necessary formula for the calculation of voltage gain, current gain, input impedance and output impedance. (7)
- Q-8 Attempt all questions (14)**
- a) What do you mean by oscillation circuit? What are the general conditions for it? (3)
 - b) Draw and explain Hartley oscillator. (4)
 - c) Draw and explain Crystal Oscillator. Where it is used? (7)

