

Enrollment No: \_\_\_\_\_ Exam Seat No: \_\_\_\_\_

# C.U. SHAH UNIVERSITY

## Summer Examination-2022

Subject Name: Circuit Theory

Subject Code: 4TE03CIT1

Branch: B.Tech (Electrical)

Semester: 3

Date: 26/04/2022

Time: 02:30 To 05:30

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
  - (2) Instructions written on main answer book are strictly to be obeyed.
  - (3) Draw neat diagrams and figures (if necessary) at right places.
  - (4) Assume suitable data if needed.
- 

- Q-1 Attempt the following questions: (14)**
- a) Unit of inductance is \_\_\_\_\_ (1)**  
a) Weber  
b) Henry  
c) Farad  
d) Tesla
- b) If the resistances  $3\Omega$ ,  $5\Omega$ ,  $7\Omega$ ,  $9\Omega$  are in series, then their equivalent resistance ( $\Omega$ ) is? (1)**  
a) 9  
b) 20  
c) 24  
d) 32
- c) Energy stored in an inductor is \_\_\_\_\_ (1)**  
a)  $LI$   
b)  $LI^2$   
c)  $LI/2$   
d)  $LI^2/2$
- d) Resistance depends on the temperature of the conductor. (1)**  
a) True  
b) False
- e) Every circuit is a network, but all networks are not circuits. (1)**  
a) True  
b) False
- f) Which of the following is not an example of a linear element? (1)**  
a) Resistor  
b) Thermistor  
c) Inductor



- d) Capacitor
- g)** Which of the following is an active element? (1)
- a) Resistor  
b) Inductor  
c) Capacitor  
d) OP-AMP
- h)** In Superposition theorem, while considering a source, all other voltage sources are? (1)
- a) open circuited  
b) short circuited  
c) change its position  
d) removed from the circuit
- i)** Mesh analysis is applicable for non-planar networks also. (1)
- a) true  
b) false
- j)** Kirchoff's voltage law is based on principle of conservation of \_\_\_\_\_ (1)
- a) energy  
b) momentum  
c) mass  
d) charge
- k)** The maximum power is delivered from a source to its load when the load resistance is \_\_\_\_\_ the source resistance. (1)
- a) greater than  
b) less than  
c) equal to  
d) less than or equal to
- l)** If the source impedance is complex, then the condition for maximum power transfer is? (1)
- a)  $Z_L = Z_S$   
b)  $Z_L = Z_S^*$   
c)  $Z_L = -Z_S$   
d)  $Z_L = -Z_S^*$
- m)** The circuit in which current has a complete path to flow is called \_\_\_\_\_ circuit. (1)
- a) short  
b) open  
c) closed  
d) open loop
- n)** If the voltage-current characteristics is a straight line through the origin, then the element is said to be? (1)
- a) Linear element  
b) Non-linear element  
c) Unilateral element  
d) Bilateral element

**Attempt any four questions from Q-2 to Q-8**

**Q-2**

**Attempt all questions**

**(14)**



- a) State and explain Norton's theorem. (7)  
 b) Write short note on Thevenin's theorem. (7)

**Q-3 Attempt all questions (14)**

- a) Write statement of superposition theorem and explain theorem with electric circuit. (7)  
 b) State and explain maximum power transfer theorem. (7)

**Q-4 Attempt all questions (14)**

- a) Briefly explain about ideal current sources and ideal voltage sources. (7)  
 b) Determine the mesh current  $I_1$  and  $I_2$  in the network of fig 1 using mesh analysis. (7)

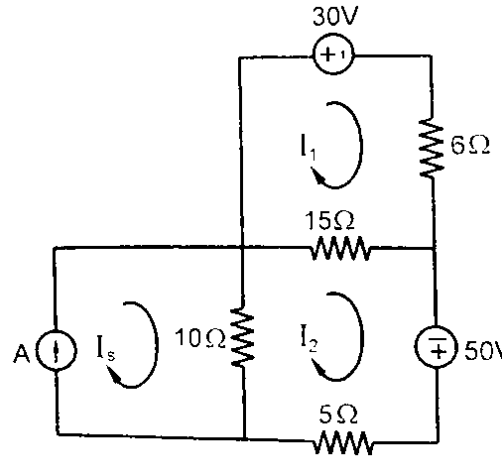


Figure : 1

**Q-5 Attempt all questions (14)**

- a) State and explain Tellegen's theorem. (7)  
 b) State and explain Kirchhoff's Current Law and Voltage Law. (7)

**Q-6 Attempt all questions (14)**

- a) State and explain initial and final value theorem. (7)  
 b) Write short note on reciprocity theorem. (7)

**Q-7 Attempt all questions (14)**

- a) Write and explain relationship between Z parameters and Y parameters. (7)  
 b) Explain the classification of Time domain and Frequency domain analysis. (7)

**Q-8 Attempt all questions (14)**

- a) Derive formulae to convert given 'Y' parameters into 'h' parameters. (7)  
 b) Explain the concept of poles and zeros and their significance. (7)

