

(A) 10 (B) 50 (c) 100 (D) 200

i) In a three-phase full converter, if load current is I and ripple free, then the average thyristor current is _____.

(A) $I/2$ (B) $I/3$ (C) $I/4$ (D) $I/5$

j) In a three-phase full converter, the output voltage is at a frequency equal to _____.

(A) supply frequency f (B) $2f$ (C) $3f$ (D) $6f$

k) The efficiency of the chopper can be expected in the range of _____%.

(A) 50 to 55 (B) 65 to 72 (c) 82 to 87 (D) 92 to 99

l) In a DC Choppers, the waveform for _____.

(A) input voltage is continuous and output voltage is discontinuous

(B) input voltage is discontinuous and output voltage is continuous

(C) input voltage and output voltage are continuous

(D) input voltage and output voltage are discontinuous

m) The effect of source inductance on the performance of the single phase and three phase full converter is to _____.

(A) reduce the ripple in the load current

(B) make discontinuous current as continuous

(C) reduce the output voltage

(D) increase the load voltage

n) In a three-phase controlled bridge rectifier, with an increase of an overlap angle, the output dc voltage _____.

(A) increases

(B) decreases

(C) does not change

(D) depends upon load inductance

Attempt any four questions from Q-2 to Q-8:

Q-2 Attempt all questions (14)

a) Illustrate the various protection scheme of power circuit. (3)

b) Illustrate the various protection scheme for gating circuit of an SCR. (4)

c) Discuss two transistor model of SCR and draw its VI Characteristics. (7)

Q-3 Attempt all questions (14)

a) Discuss Safe Operating Areas for MOSFET. (3)

b) Discuss Safe Operating Areas for IGBT. (4)

c) Give a general comparison of power semiconductor devices for Thyristor, TRIAC, power-MOSFET & IGBT. (7)

Q-4 Attempt all questions (14)

a) Draw basic structure, symbol and output characteristics of an IGBT. (3)

b) Explain the operation of NPN-type Power BJT in CE-mode. (4)

c) Write a comprehensive technical note on MCT (7)



