



sheet. Explain any two.

- (a) State the characteristics of an ideal opamp (7)
- Q-4 Attempt all questions (14)**
- (a) State and explain equivalent circuit of an opamp. (7)
- (b) Explain the inverting mode operation of opamp with negative feedback (7)
- Q-5 Attempt all questions (14)**
- (a) Derive the equation of closed loop voltage gain for inverting configuration with feedback. (7)
- (b) State the name of any five parameters those are listed on opamp data sheet. Explain any two. (7)
- Q-6 Attempt all questions (14)**
- (a) Discuss the closed loop frequency response of an opamp. (7)
- (b) Discuss the low voltage a.c. voltmeter application using opamp. (7)
- Q-7 Attempt all questions (14)**
- (a) Discuss the operation of summing amplifier using opamp. (7)
- (b) Discuss the operation of integrator using opamp. (7)
- Q-8 Attempt all questions (14)**
- (a) Briefly discuss about the following: (a) Gain bandwidth product (b) Slew rate (c) Common mode rejection ratio. (7)
- (b) Discuss the operation of first order filter using an opamp. (7)

